
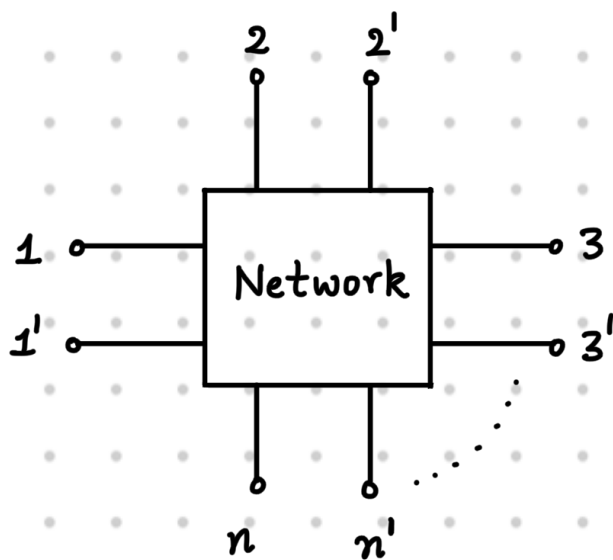


Network Functions

A port is a pair of terminals connecting an electrical network/circuit to an external circuit, as a point of entry or exit for charge.

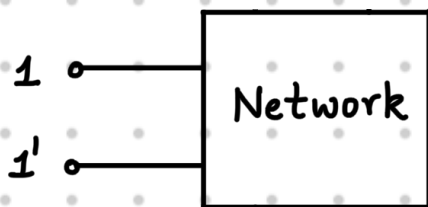A one-port network, a two-port network and a general n -port network is shown below.



(We will limit our discussion to 1-port and 2-port networks.)

The input port is generally connected to an energy source, which forms the driving force for the network. The output port is generally connected to a load.


We shall now define some network functions that are commonly used in network theory.

Transform Impedance: Defined as the ratio of the voltage transform to the current transform at a port of a network with zero initial conditions and no independent sources. This quantity is also called as driving-point impedance.

That is,

$$Z(s) = \frac{V_1(s)}{I_1(s)}$$

↓
at port 1-1'

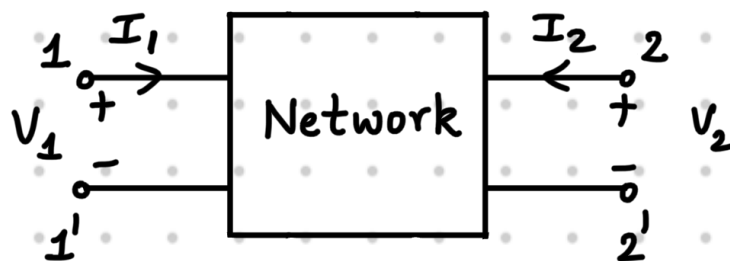

Transform Admittance: Defined as the ratio of the current transform to the voltage transform at a port of a network with zero initial conditions and no independent sources. This quantity is also called as driving-point admittance.

$$Y(s) = \frac{I_1(s)}{V_1(s)} = \frac{1}{Z(s)}$$

↓
at port 1-1'

Voltage Transfer Function: Defined as the ratio of one voltage to another voltage.

Example: $G_{21}(s) = \frac{V_2(s)}{V_1(s)}$

Current Transfer Function: Defined as the ratio of one current to another current.

Example: $\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}$


Transfer Impedance Function: Defined as the ratio of one voltage to another current.

Example: $Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$


Transfer Admittance Function: Defined as the ratio of one current to another voltage.

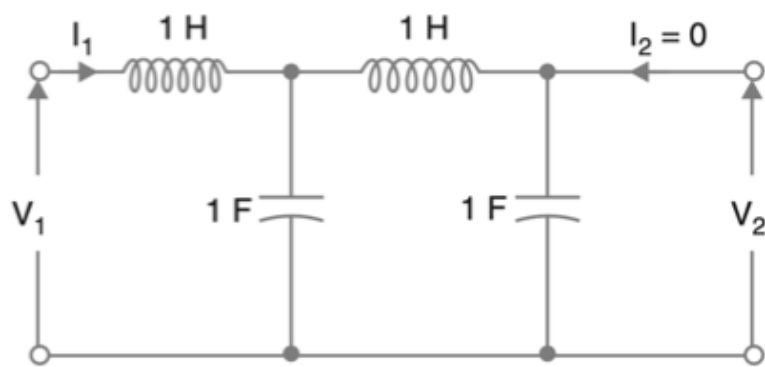Example: $Y_{21}(s) = \frac{I_1(s)}{V_2(s)}$

Q. Find the driving-point impedance at the input port of :



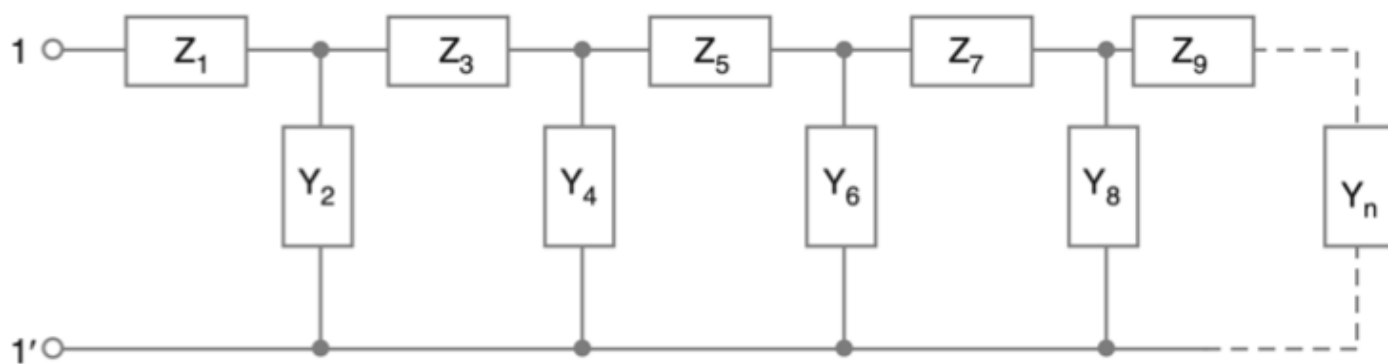A. For a general ladder network, the driving-point impedance is given as:




$$Z = Z_1 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_4 + \dots}}}$$

Hence, for our network: $Z = s + \frac{1}{s + \frac{1}{s + \frac{1}{s}}}$
 at input port

$$\text{Hence, } Z = \frac{s^4 + 3s^2 + 1}{s^3 + 2s}$$

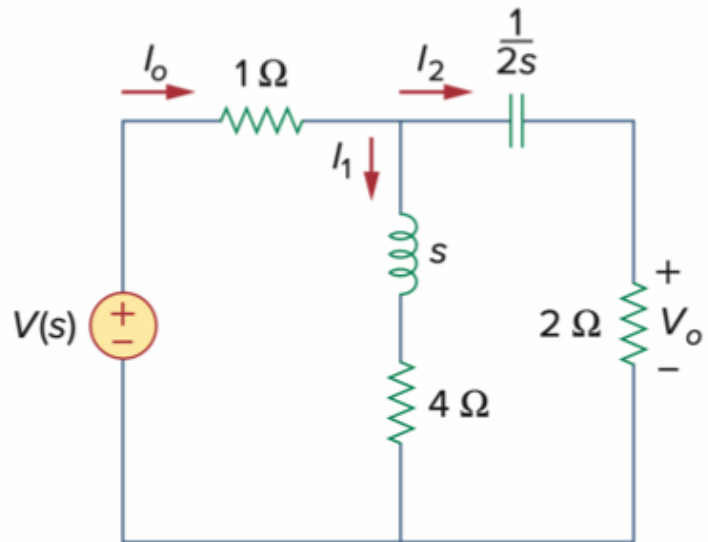Q. Calculate the transfer function $\frac{V_o(s)}{I_o(s)}$ of the circuit :




$$A. \quad \frac{V_o(s)}{I_o(s)} = \frac{2 I_2(s)}{I_o(s)}$$

$$= 2 \left(\frac{4 + s}{4 + s + \frac{1}{2s} + 2} \right)$$

$$\Rightarrow \frac{V_o(s)}{I_o(s)} = \frac{4s(s+4)}{2s^2 + 12s + 1}$$

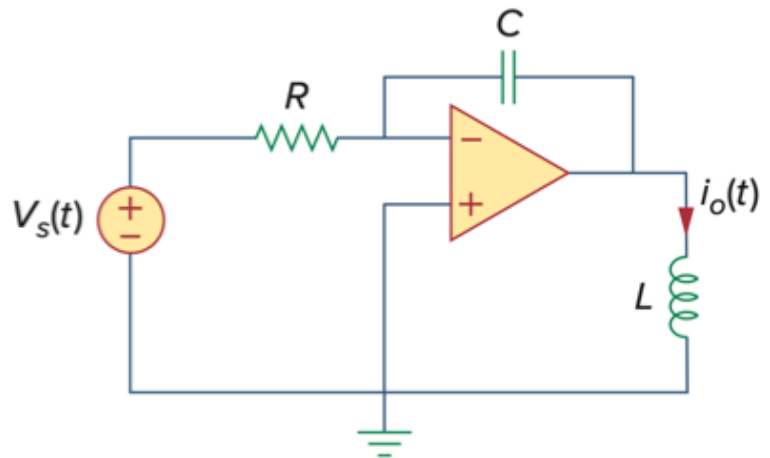Q. Calculate the transfer function $\frac{I_o(s)}{V_s(s)}$ of the circuit :




$$A. \quad \frac{V_s(s) - 0}{R} = \frac{0 - V_o(s)}{\frac{1}{Cs}}$$

$$\text{and} \quad I_o(s) = \frac{V_o(s)}{sL}$$

$$\Rightarrow \quad \frac{I_o(s)}{V_s(s)} = \frac{-1}{(RLCs^2)}$$

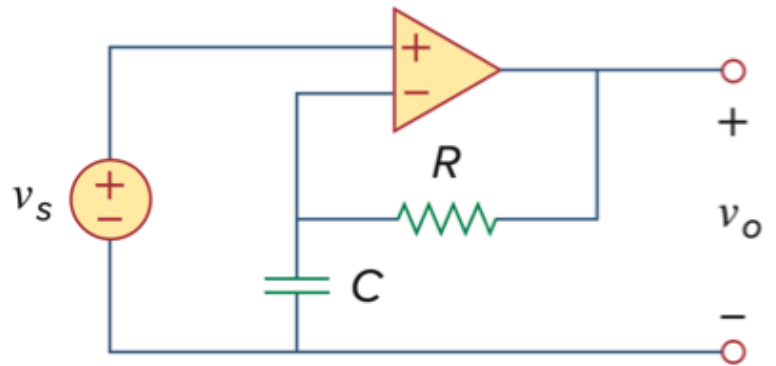Q. Calculate the transfer function $\frac{V_o(s)}{V_s(s)}$ of the circuit :



A.
$$\frac{V_o(s) - V_s(s)}{R} = \frac{V_s(s)}{\frac{1}{Cs}}$$

$$\Rightarrow \frac{V_o(s)}{V_s(s)} = 1 + sRC$$