

## 2. Analysis of Electrical Networks :

Electrical networks may be analyzed by writing the integro-differential equation(s) of the system and then solving these equations by the Laplace transform. However, it is also possible to analyze electrical networks directly without having to write the integro-differential equations.

For this purpose, we need to represent a network in the "frequency domain" where all the voltages and currents are represented by their Laplace transforms.

$$v(t) = i R \Rightarrow V(s) = I(s) R$$

$$v(t) = L \frac{di}{dt} \Rightarrow V(s) = L (s I(s) - i(0^-))$$




$$i(t) = C \frac{dv}{dt} \Rightarrow I(s) = C (s V(s) - v(0^-))$$

$$\sum_{j=1}^k v_j(t) = 0 \Rightarrow \sum_{j=1}^k V_j(s) = 0$$




$$\sum_{j=1}^m i_j(t) = 0 \Rightarrow \sum_{j=1}^m I_j(s) = 0$$
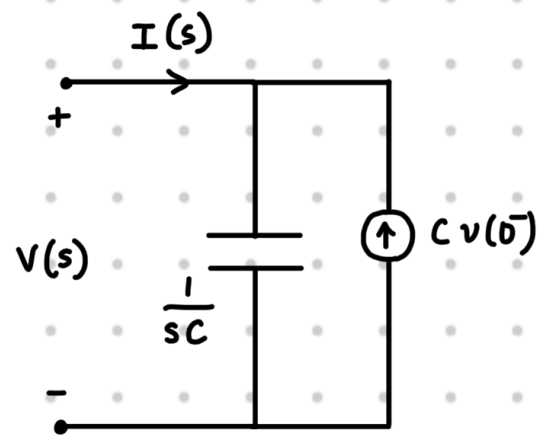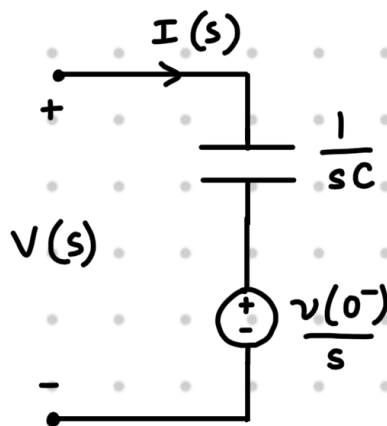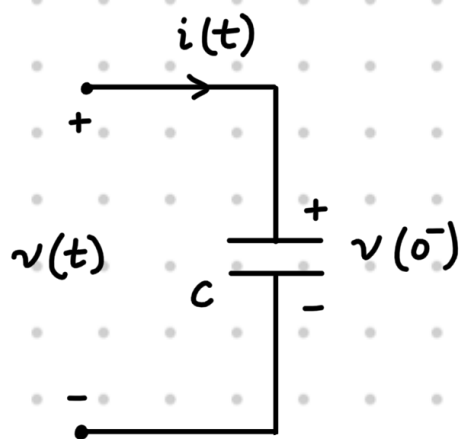
## Initial condition generators

Equivalent representation of a Capacitor with initial voltage:




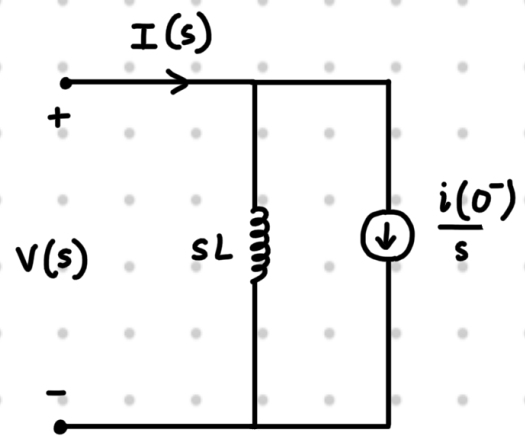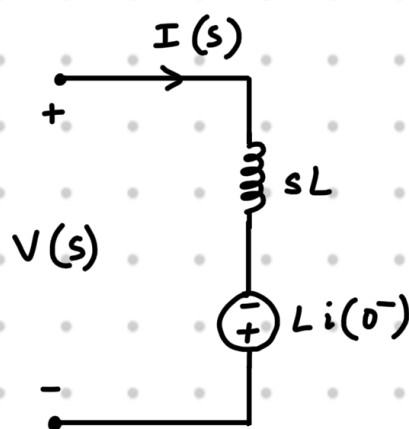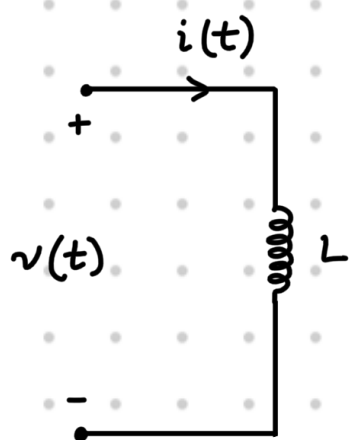Equivalent representation of an Inductor with initial current:


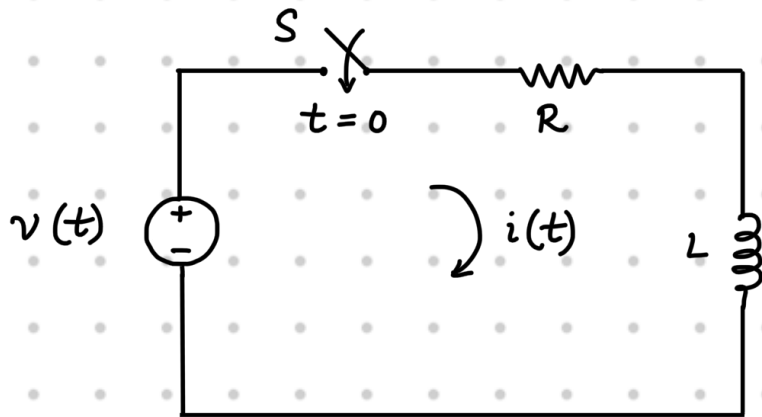
## Series R-L circuit

Let the switch  $S$  be closed at time  $t=0$  for the RL circuit shown below.



Applying Kirchhoff's voltage law,

$$v(t) = R i(t) + L \frac{di}{dt}$$

Taking Laplace transform,

$$V(s) = R I(s) + L \{s I(s) - i(0^-)\}$$

With  $i(0^-) = i(0^+) = 0$ ,

$$\Rightarrow V(s) = (R + sL) I(s)$$

Step Response :

If  $v(t) = V_0 u(t)$ , then  $V(s) = \frac{V_0}{s}$

$$\Rightarrow \frac{V_0}{s} = (R + sL) I(s)$$

$$\Rightarrow I(s) = \frac{V_0}{L} \cdot \frac{1}{s(s + \frac{R}{L})} = \frac{V_0}{R} \left( \frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$

Therefore,  $i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right) u(t)$

Impulse Response:


If  $v(t) = \delta(t) \Rightarrow V(s) = 1$

$$\Rightarrow 1 = (R + sL) I(s)$$

$$\Rightarrow I(s) = \frac{1}{L} \left( \frac{1}{s + R/L} \right) \Rightarrow i(t) = \frac{1}{L} e^{-\frac{Rt}{L}} u(t)$$

Series R-C circuit

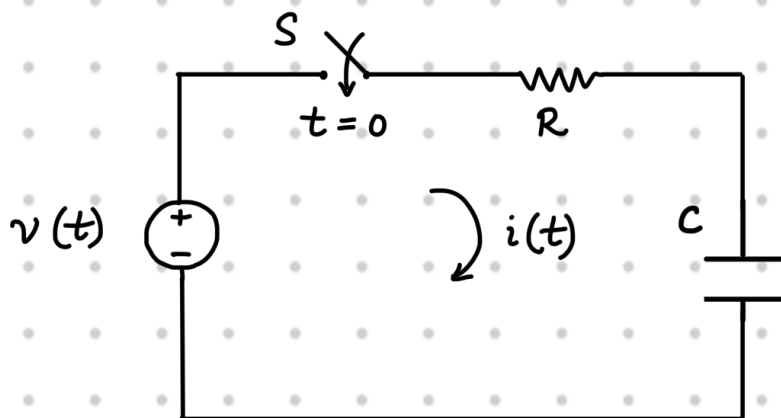Let the switch  $S$  be closed at time  $t=0$  for the RC circuit shown below.



$$\text{Then, } v(t) = R i(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$\Rightarrow v(t) = R i(t) + \frac{1}{C} \int_0^t i(t) dt + \frac{1}{C} \int_{-\infty}^0 i(t) dt$$

Taking Laplace transform,

$$V(s) = R I(s) + \frac{1}{C} \left[ \frac{I(s)}{s} + \frac{q(0^-)}{s} \right]$$

$$\text{With } q(0^-) = q(0^+) = 0$$

$$\Rightarrow V(s) = \left( R + \frac{1}{sC} \right) I(s)$$

Step Response :

$$\text{If } v(t) = V_0 u(t), \text{ then } V(s) = \frac{V_0}{s}$$

$$\Rightarrow \frac{V_0}{s} = \left( R + \frac{1}{sC} \right) I(s) \Rightarrow I(s) = \frac{V_0/R}{s + \frac{1}{RC}}$$

$$\text{Therefore, } i(t) = \frac{V_0}{R} e^{-t/RC} u(t)$$

Impulse Response :


$$\text{If } v(t) = \delta(t) \Rightarrow V(s) = 1$$

$$\Rightarrow 1 = \left( R + \frac{1}{sC} \right) I(s) \Rightarrow I(s) = \frac{s}{R \left( s + \frac{1}{RC} \right)}$$


$$\Rightarrow I(s) = \frac{1}{R} \left[ 1 - \frac{1}{RC} \frac{1}{(s + 1/RC)} \right]$$

$$\text{Therefore, } i(t) = \frac{1}{R} \left[ \delta(t) - \frac{1}{RC} e^{-t/RC} u(t) \right]$$

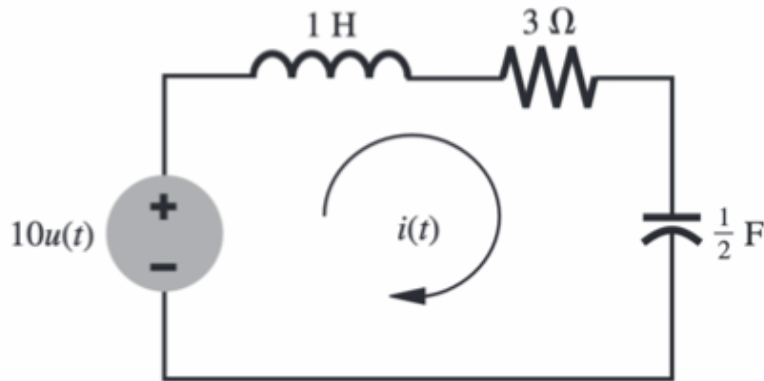Q. Find the loop current  $i(t)$  in the circuit shown below if all the initial conditions are zero.



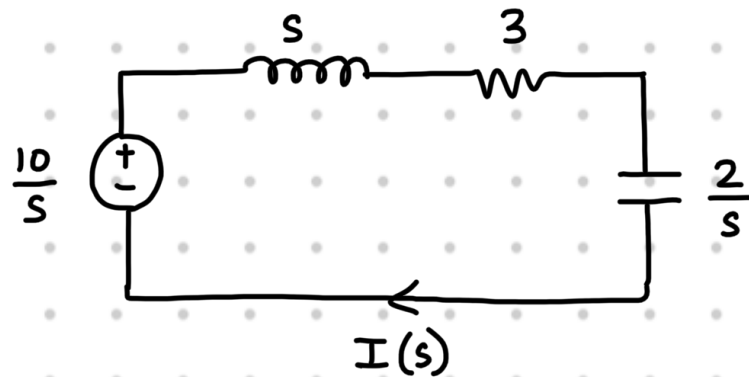A. The equivalent circuit in the  $s$ -domain is:



The total impedance in the loop is:

$$Z(s) = s + 3 + \frac{2}{s} = \frac{s^2 + 3s + 2}{s}$$

$$\Rightarrow I(s) = \frac{V(s)}{Z(s)} = \frac{10/s}{\frac{s^2 + 3s + 2}{s}} = \frac{10}{s+1} - \frac{10}{s+2}$$

$$\Rightarrow i(t) = 10(e^{-t} - e^{-2t})u(t)$$