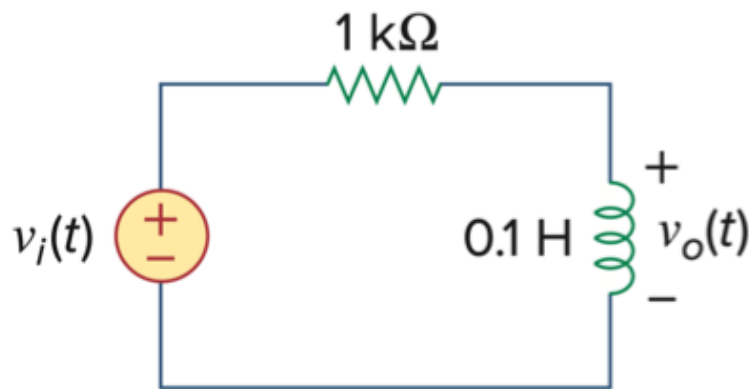


Q. What type of filter is shown below?  
What is the cutoff / corner frequency?



$$A. \quad H(s) = \frac{V_o(s)}{V_i(s)} = \frac{sL}{R + sL}$$

$$\Rightarrow H(j\omega) = \frac{j\omega L}{R + j\omega L}$$

$$\Rightarrow |H(j\omega)| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}}$$

Clearly,  $|H(0)| = 0$ ,  $|H(\infty)| = 1$


Hence, this is a high-pass filter.

The cut-off frequency  $\omega_c = \frac{R}{L} = 10^4 \text{ rad/s}$ .

Q. What type of filter is shown below?

What is the cutoff / corner frequency?

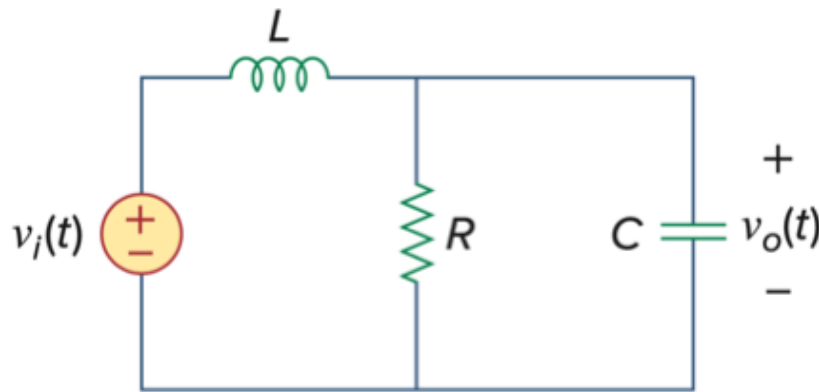Use  $R = 2\text{k}\Omega$ ,  $L = 2\text{H}$ , and  $C = 2\mu\text{F}$ .



$$A. \quad H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R}{s^2 RLC + sL + R}$$

$$\Rightarrow |H(j\omega)| = \frac{R}{\sqrt{(R - \omega^2 RLC)^2 + \omega^2 L^2}}$$

✓

$$H(0) = 1 \quad \text{and} \quad H(\infty) = 0$$

Hence, this is a second-order low pass filter.

Solving  $\omega_c$  for cut-off frequency,

$$\omega_c^2 \approx 0.55 \times 10^6 \Rightarrow \omega_c \approx 742 \text{ rad/sec}$$

Q. Design a band-stop filter to reject a 200 Hz sinusoid while passing other frequencies and with a bandwidth of 100 Hz. (Use  $R = 150 \Omega$ ).

A. For an RLC band-stop filter,

$$|H(j\omega)| = \frac{(\omega L - 1/\omega C)}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

Calculating half-power frequencies,

$$P_\omega = \frac{1}{2} P_{\max} \Rightarrow \frac{R}{R^2 + (\omega L - 1/\omega C)^2} = \frac{1}{2R}$$

$$\Rightarrow \omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \left( \begin{array}{l} \text{negative roots} \\ \text{rejected} \end{array} \right)$$


$$\text{and } \omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{Hence, } B = \omega_2 - \omega_1 = \frac{R}{L} \quad \text{and } \omega_0 = \frac{1}{\sqrt{LC}}$$

Substituting the values,  $C \approx 2.65 \mu F$

and  $L \approx 240 \text{ mH}$

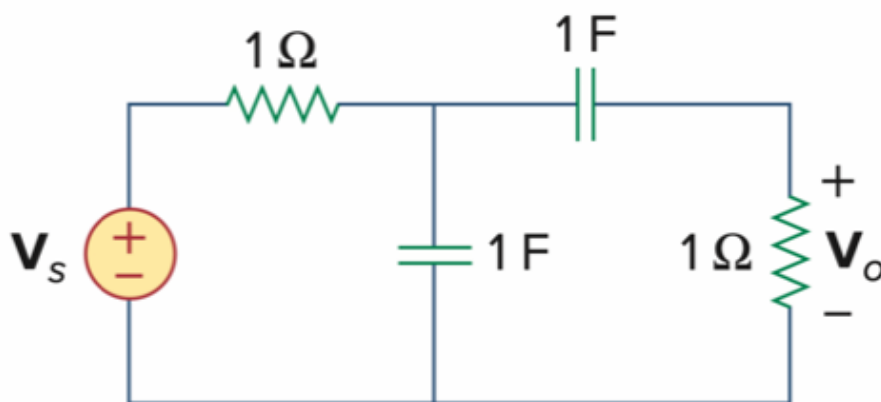Q. What type of filter is shown below?  
What is the center frequency and BW?



A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{sRC}{1 + 3sRC + s^2R^2C^2}$$

$$= \frac{1}{3} \left[ \frac{\frac{3}{RC} s}{s^2 + \frac{3}{RC} s + \frac{1}{R^2C^2}} \right] \rightarrow \text{Band-Pass Filter}$$


Comparing the equation with  $K \left( \frac{Bs}{s^2 + Bs + \omega_0^2} \right)$

given  $R = 1\Omega$ ,  $C = 1F$

$$\omega_0^2 = \frac{1}{R^2C^2} \Rightarrow \omega_0 = 1 \text{ rad/sec}$$

$$B = \frac{3}{RC} = 3 \text{ rad/sec.}$$

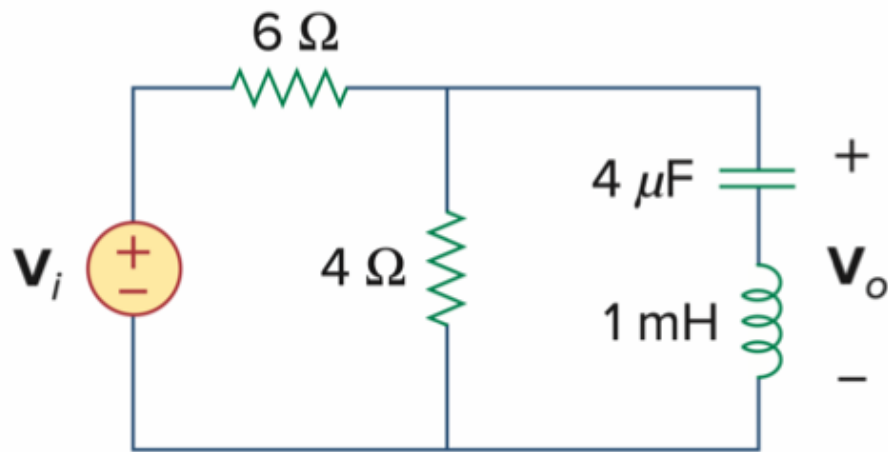Q. What type of filter is shown below?  
What is the center frequency and BW?



A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_1(1 + s^2 LC)}{(R_1 + R_2) + s R_1 R_2 C + s^2 LC(R_1 + R_2)}$$

$$= \frac{R_1}{R_1 + R_2} \frac{\left(s^2 + \frac{1}{LC}\right)}{\left(s^2 + \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{L} s + \frac{1}{LC}\right)} \rightarrow \text{Band-Stop Filter}$$


Comparing the equation with  $K \left( \frac{s^2 + \omega_0^2}{s^2 + Bs + \omega_0^2} \right)$

given  $R_1 = 4\Omega$ ,  $R_2 = 6\Omega$ ,  $C = 4\mu F$ ,  $L = 1mH$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 \approx 15.8 \text{ krad/sec}$$

$$B = \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{L} = 2.4 \text{ krad/sec}$$

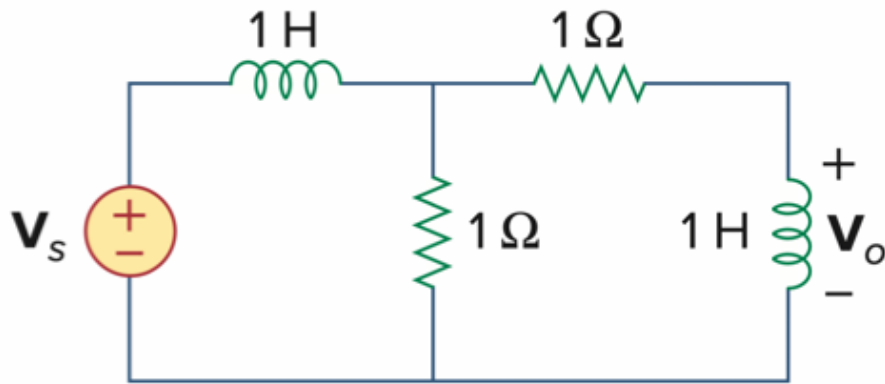Q. What type of filter is shown below?  
What is the center frequency and BW?



A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{sRL}{R^2 + 3sRL + s^2L^2}$$

$$= \frac{1}{3} \left[ \frac{3 \frac{R}{L} s}{s^2 + 3 \frac{R}{L} s + \frac{R^2}{L^2}} \right] \rightarrow \text{Band-Pass Filter}$$

Comparing the equation with  $K \left( \frac{Bs}{s^2 + Bs + \omega_0^2} \right)$

given  $R = 1\Omega$ ,  $L = 1\text{H}$

$$\omega_0^2 = \frac{R^2}{L^2} \Rightarrow \omega_0 = 1 \text{ rad/sec}$$

$$B = 3 \frac{R}{L} = 3 \text{ rad/sec}$$