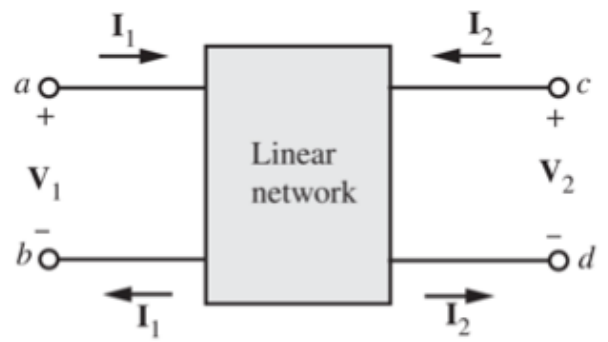


Y / Admittance / Short-circuit Parameters

$$(I_1, I_2) = f(V_1, V_2)$$

$$\Rightarrow [I] = [Y][V]$$



$$\text{or } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\text{Hence, } I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$\text{Then, } y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}, \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

short-circuit
input admittance


short-circuit reverse
transfer admittance

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}, \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$



short-circuit forward
transfer admittance

short-circuit
output admittance

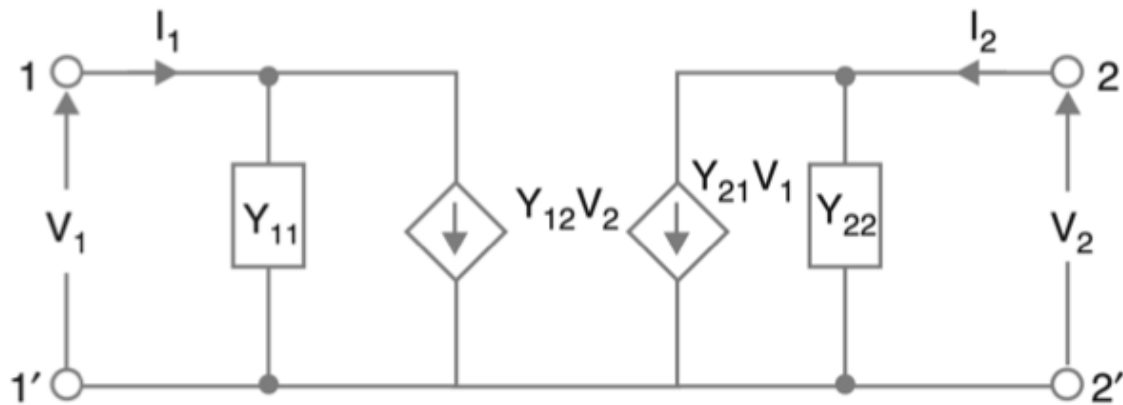The equivalent circuit representation is given below with $Y_{12}V_2$ and $Y_{21}V_1$ as VCCS.



Condition for Reciprocity & Symmetry:

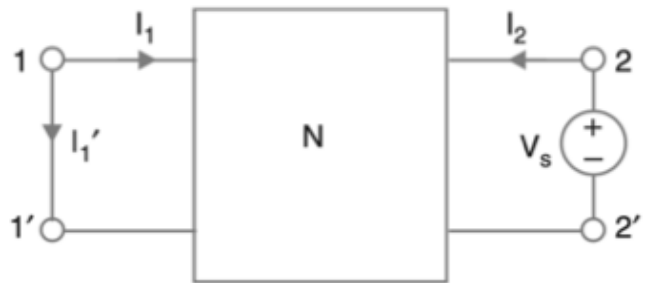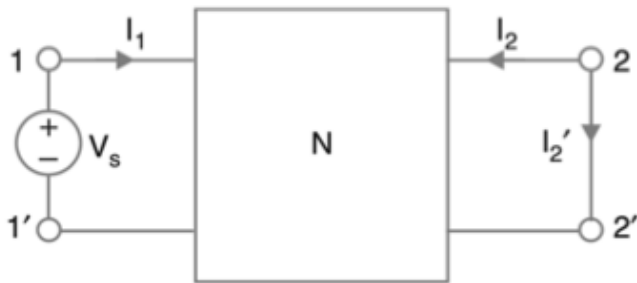

For reciprocity,

$$I_1' = I_2' \Rightarrow -V_s Y_{12} = -V_s Y_{21}$$

$$\Rightarrow \underline{\underline{Y_{12} = Y_{21}}}$$

For symmetry (the ports can be interchanged without changing the port voltages and currents)

$$\Rightarrow \left. \frac{I_1}{V_1} \right|_{V_2=0} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \Rightarrow \underline{\underline{Y_{11} = Y_{22}}}$$

Matrix Partitioning for Y parameters :

For a two-port network, the KCL/Nodal equations are : $[Y][V] = [I]$

$$Y_{11} V_1 + Y_{12} V_2 + \dots + Y_{1n} V_n = I_1$$

$$Y_{21} V_1 + Y_{22} V_2 + \dots + Y_{2n} V_n = I_2$$

$$\text{or } Y_{31} V_1 + Y_{32} V_2 + \dots + Y_{3n} V_n = 0$$

\vdots

$$Y_{n1} V_1 + Y_{n2} V_2 + \dots + Y_{nn} V_n = 0$$

$$\Rightarrow \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & \dots & Y_{1n} \\ Y_{21} & Y_{22} & \dots & \dots & Y_{2n} \\ Y_{31} & \vdots & \vdots & \vdots & \vdots \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Y_{n1} & \vdots & \vdots & \vdots & Y_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

Hence,


$$\begin{bmatrix} M & N \\ P & Q \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

which can be simplified as,

$$[M - NQ^{-1}P] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Q. Determine the Y -parameters of :

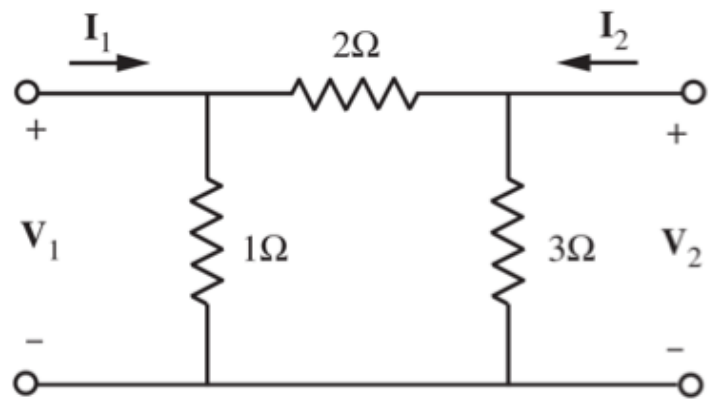Furthermore, if a $2A$ source is connected at the input, find the current through a 4Ω load at the output.



A. Writing the KCL equations,

$$\begin{bmatrix} 3/2 & -1/2 \\ -1/2 & 5/6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Hence,


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{3}{2} \Omega^{-1}, \quad Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -\frac{1}{2} \Omega^{-1}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{1}{2} \Omega^{-1}, \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{5}{6} \Omega^{-1}$$

$$\Rightarrow I_1 = \frac{3}{2} V_1 - \frac{1}{2} V_2 \quad \text{and} \quad I_2 = -\frac{1}{2} V_1 + \frac{5}{6} V_2$$

$$\text{If } I_1 = 2A \Rightarrow I_2 = -\frac{2}{11} A$$

Q. Determine the Y -parameters of :

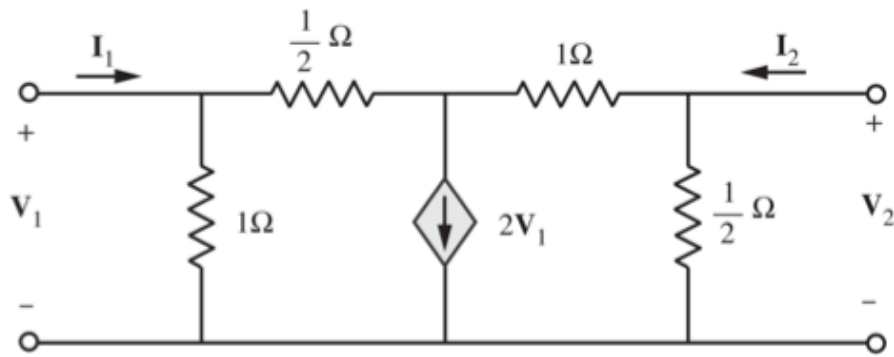

A. Writing the KCL equations,

$$3V_1 - 2V_3 = I_1$$

$$V_2 - 3V_3 = 0$$

$$3V_2 - V_3 = I_2$$

$$\Rightarrow 9V_1 - 2V_2 = 3I_1$$


$$8V_2 = 3I_2$$

Hence,

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 3 \Omega^{-1}, \quad Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -\frac{2}{3} \Omega^{-1}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = 0 \Omega^{-1}, \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{8}{3} \Omega^{-1}$$

Q. Determine the Y -parameters of :

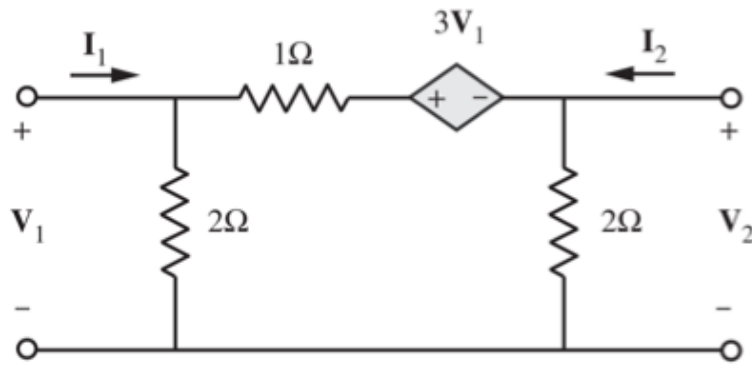

A. Writing the KCL equations,

$$\frac{V_1}{2} + \frac{V_2}{2} = I_1 + I_2$$

$$-\left(\frac{3V_1}{2} + V_2\right) = I_1$$


Hence,

$$\begin{bmatrix} -\frac{3}{2} & -1 \\ 2 & \frac{3}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = -\frac{3}{2} \Omega^{-1}, \quad Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -1 \Omega^{-1}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = 2 \Omega^{-1}, \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{3}{2} \Omega^{-1}$$

Q. Determine the γ -parameters of :

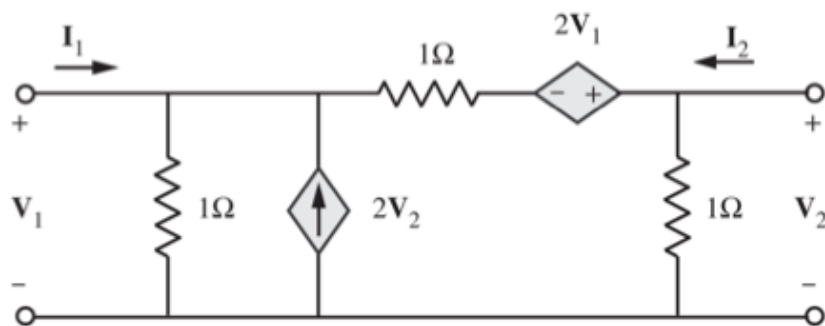

A. Writing the KCL equations,

$$V_1 - V_2 = I_1 + I_2$$

$$4V_1 - 3V_2 = I_1$$


Hence,

$$\begin{bmatrix} 4 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 4 \Omega^{-1}, \quad Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -3 \Omega^{-1}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -3 \Omega^{-1}, \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = 2 \Omega^{-1}$$

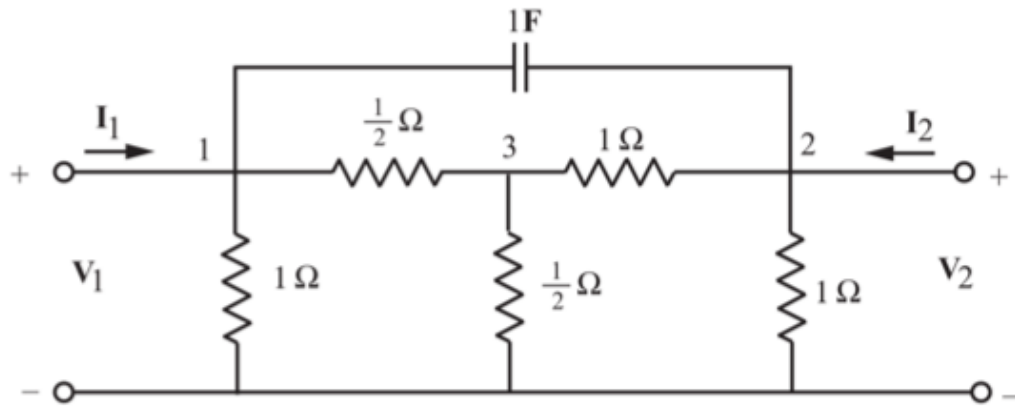Q. Determine the y -parameters (s -domain) of :



A. Writing the KCL equations,

$$\begin{bmatrix} 3+s & -s & -2 \\ -s & 2+s & -1 \\ -2 & -1 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ 0 \end{bmatrix}$$

Simplifying,

$$\left(s + \frac{11}{5}\right) V_1 - \left(s + \frac{2}{5}\right) V_2 = I_1$$


$$-(5s+2)V_1 + (5s+9)V_2 = 5I_2$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = s+2.2, \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -(s+0.4)$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -(s+0.4), \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = s+1.8$$

Note: We can also solve this using $Z = P-QN^{-1}M$

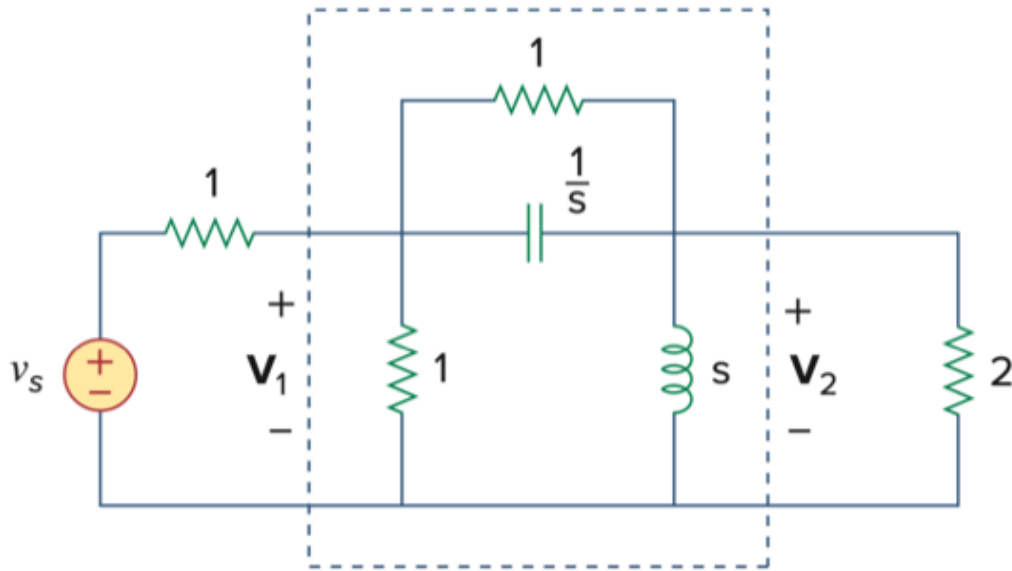Q. Determine the y -parameters (s -domain) of :



$$A. \quad y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = s + 2,$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -(s + 1),$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -(s + 1),$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{s^2 + s + 1}{s}$$

Hence, $[y] = \begin{bmatrix} s + 2 & -(s + 1) \\ -(s + 1) & \frac{s^2 + s + 1}{s} \end{bmatrix}$