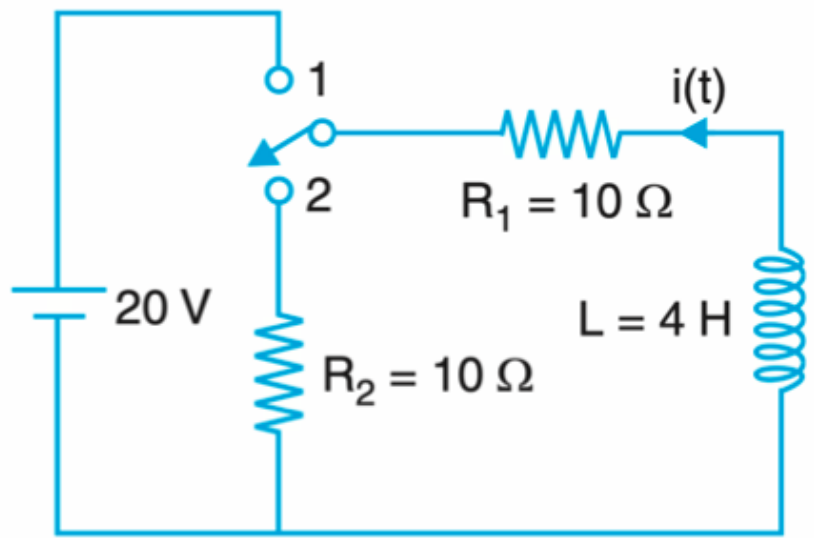



Q. In the circuit shown below, the switch is thrown from position 1 to 2 at time  $t=0$  after being in steady-state for long time. Find the energy dissipated in  $R_1$  from  $t=0$  to  $t=200\text{ ms}$ .



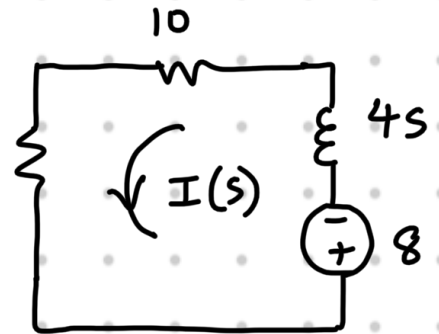A. Writing the KVL equation in the Laplace domain,

$$(20 + 4s) I(s) = -4(2) \quad 10$$

$$\Rightarrow I = \frac{-8}{4s + 20} = \frac{-2}{s + 5}$$




$$\Rightarrow i(t) = \mathcal{L}^{-1}\left(\frac{-2}{s+5}\right) = -2e^{-5t} \text{ A}$$


$$\text{Energy dissipated by } 10\ \Omega \text{ resistor} = \int_{t_1}^{t_2} i^2 R_1 dt$$

$$= 40 \left. \frac{e^{-10t}}{-10} \right|_0^{0.2} \approx 3.46 \text{ J}$$

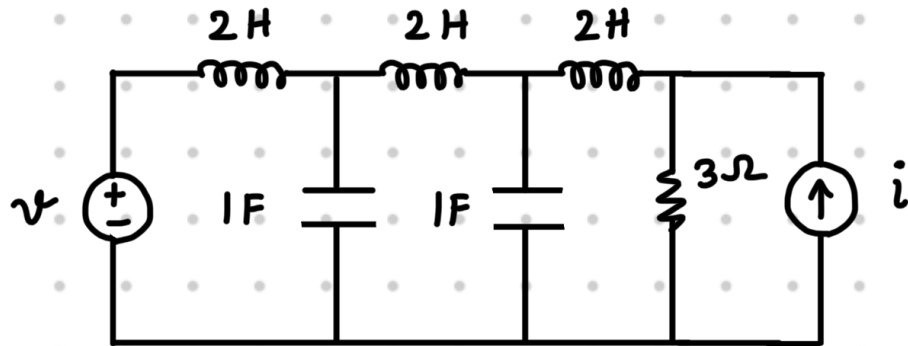Q. For the network shown below, write the KCL and KVL matrix equations in the Laplace transformed domain. (Assume zero initial conditions)




A. The KCL equations of the network.

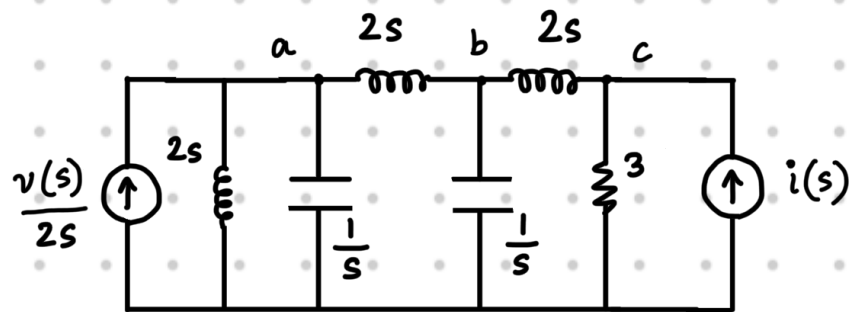

$$\begin{bmatrix} \frac{1}{2s} + \frac{1}{2s} + s & -\frac{1}{2s} & 0 \\ -\frac{1}{2s} & \frac{1}{2s} + \frac{1}{2s} + s & -\frac{1}{2s} \\ 0 & -\frac{1}{2s} & \frac{1}{2s} + \frac{1}{3} \end{bmatrix} \begin{bmatrix} v_a(s) \\ v_b(s) \\ v_c(s) \end{bmatrix} = \begin{bmatrix} \frac{v(s)}{2s} \\ 0 \\ i(s) \end{bmatrix}$$

The KVL equations of the network:

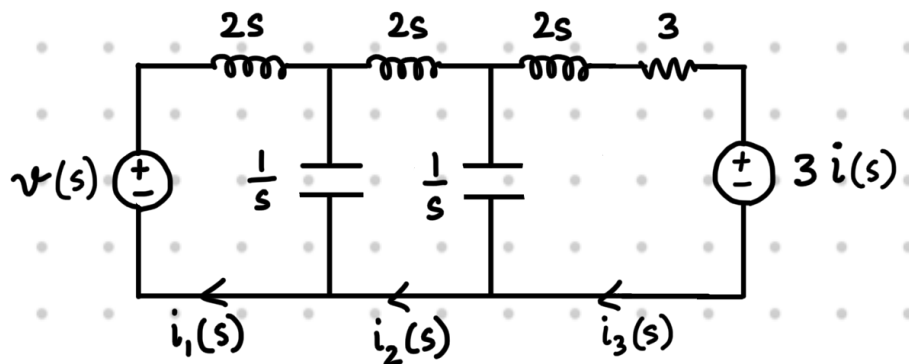


$$\begin{bmatrix} 2s + \frac{1}{s} & -\frac{1}{s} & 0 \\ -\frac{1}{s} & 2s + \frac{2}{s} & -\frac{1}{s} \\ 0 & -\frac{1}{s} & 3 + 2s + \frac{1}{s} \end{bmatrix} \begin{bmatrix} i_1(s) \\ i_2(s) \\ i_3(s) \end{bmatrix} = \begin{bmatrix} v(s) \\ 0 \\ -3i(s) \end{bmatrix}$$


Q. In the circuit shown below, the switch is thrown from position 1 to 2 at time  $t=0$ .

Given  $i_L(0^-) = 2A$ ,  
 $v_C(0^-) = 2V$ , find the  
 current  $i(t)$  for  $t > 0$ .

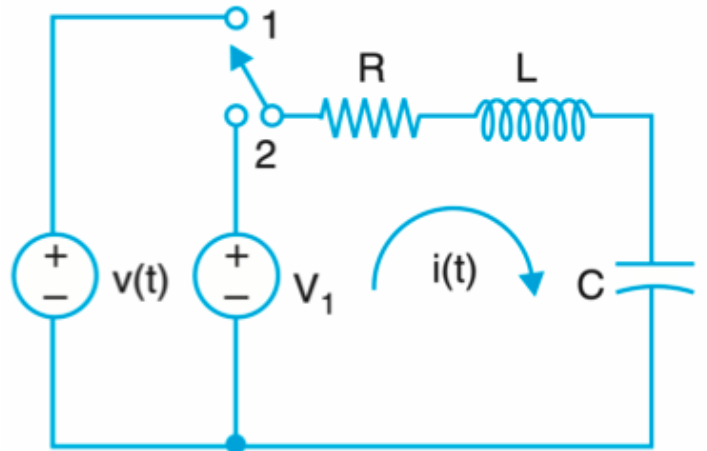Use  $L = 1H$ ,  $R = 3\Omega$ ,  
 $C = 0.5F$  and  $V_1 = 5V$ .



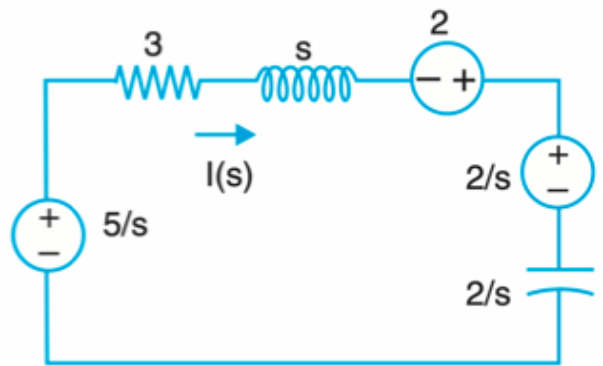A. Transforming the  
 circuit into Laplace  
 domain and writing KVL,




$$\left(3 + s + \frac{2}{s}\right) I = \left(\frac{5}{s} + 2 - \frac{2}{s}\right)$$

$$\Rightarrow I = \frac{2s + 3}{s^2 + 3s + 2} = \frac{2s + 3}{(s + 2)(s + 1)}$$


$$\Rightarrow i(t) = \mathcal{L}^{-1}\left(\frac{2s + 3}{(s + 2)(s + 1)}\right) = e^{-t} + e^{-2t}; \quad t \geq 0$$

Q. In the circuit shown below, the switch is closed at time  $t=0$ .

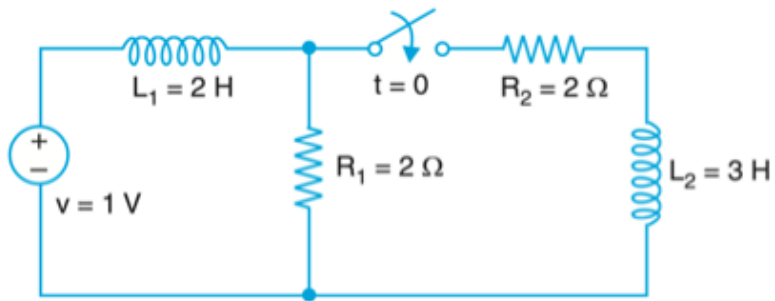Determine the current in the  $3H$  inductor.



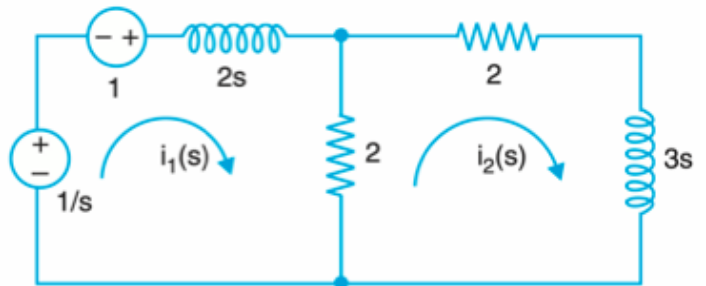A. Writing the KVL equations for the transformed network in the matrix form,



$$\begin{bmatrix} 2 + 2s & -2 \\ -2 & 4 + 3s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{s} + 1 \\ 0 \end{bmatrix}$$

Using Cramer's rule,

$$I_2 = \frac{1}{2s} - \frac{2}{5s + \frac{5}{3}} - \frac{1}{10(s+2)}$$

Therefore,  $i_2(t) = \left( \frac{1}{2} - \frac{1}{10} e^{-2t} - \frac{2}{5} e^{-\frac{t}{3}} \right) u(t)$