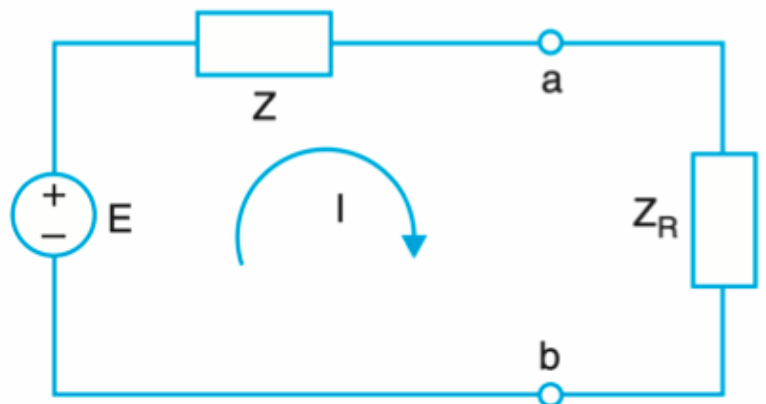


Maximum Power Transfer Theorem:

The maximum amount of power will be dissipated by a load impedance when that load impedance is the complex conjugate of the Thevenin/Norton impedance of the source network.

Suppose we have a network as shown with $Z = R + jX$ and $Z_R = R_R + jX_R$



Then, the power delivered to the load is:

$$P = I^2 R_R = \left[\frac{E}{\sqrt{(R_R + R)^2 + (X_R + X)^2}} \right]^2 R_R$$

$$\text{For maximum power, } \frac{\partial P}{\partial R_R} = \frac{\partial P}{\partial X_R} = 0$$


$$\Rightarrow R_R = R \quad \text{and} \quad X_R = -X$$

$$\Rightarrow Z_R = R - jX = (R + jX)^* = Z^*$$

Hence, for maximum power transfer, $Z_R = Z^*$

$$\text{and } P_{\max} = \frac{E^2}{4R_R}$$

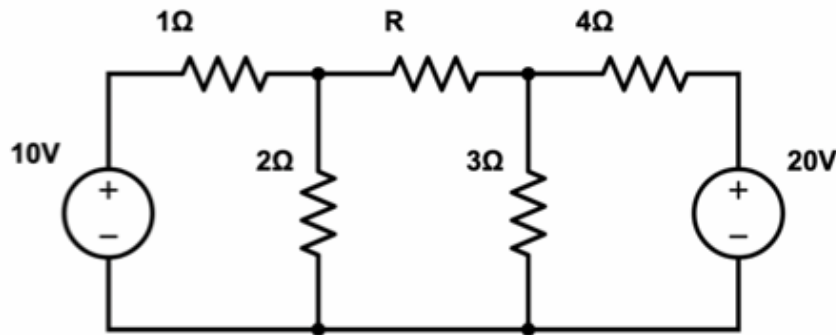Q. Find the value of R for which the power transferred across R is maximum. Calculate that maximum power transferred.




A. Calculating V_{TH} and Z_{TH} across R :

$$V_{TH} = \frac{10}{3}(2) - \frac{20}{7}(3) = -1.9V$$

$$Z_{TH} = \frac{1(2)}{1+2} + \frac{3(4)}{3+4} = 2.381\Omega$$

Hence, using the Thevenin's equivalent:

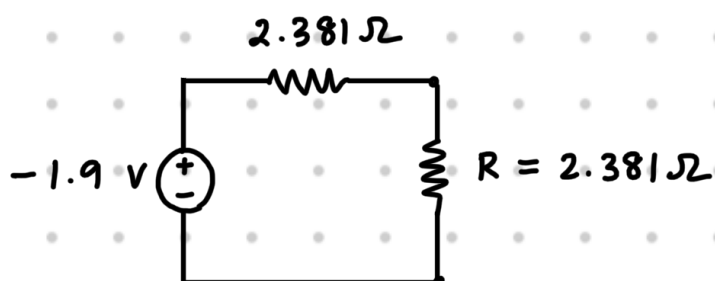
$R = 2.381\Omega$ for maximum power transfer





$$I = \frac{1.9}{(2.381) \cdot 2} = 0.4A$$

$$\Rightarrow P_R = (0.4)^2 (2.381) = 0.381W$$

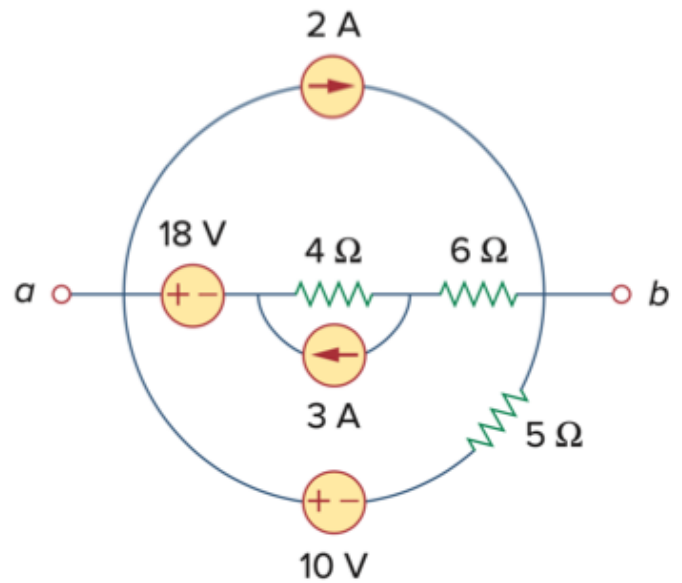Q. Find the value of impedance to be connected across the terminals a-b for which the power transferred across it is maximum. Calculate that maximum power transferred.




A. Using source transformations,

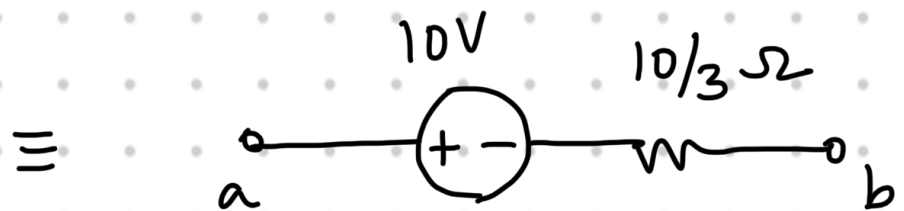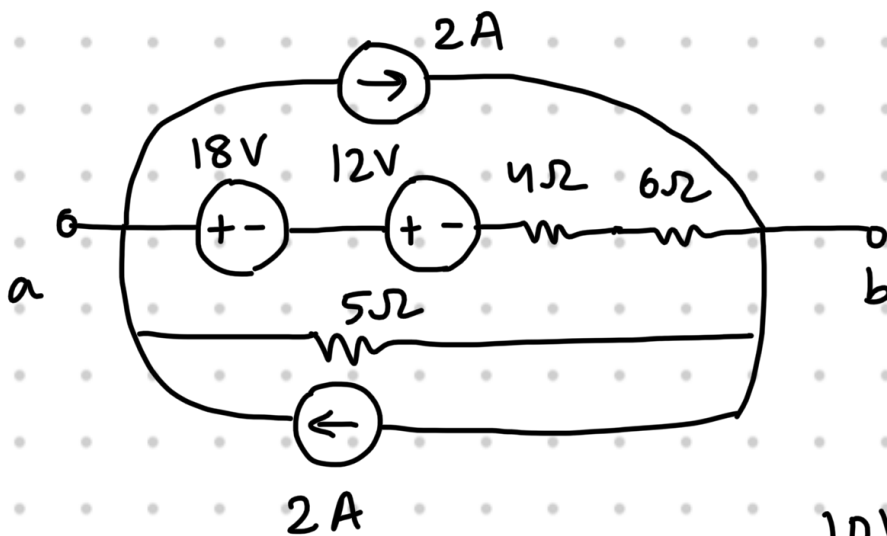

Hence, $R_L = \frac{10}{3} \Omega$

and $P_{\max} = \frac{100}{4 \cdot \frac{10}{3}} = 7.5 \text{ W}$

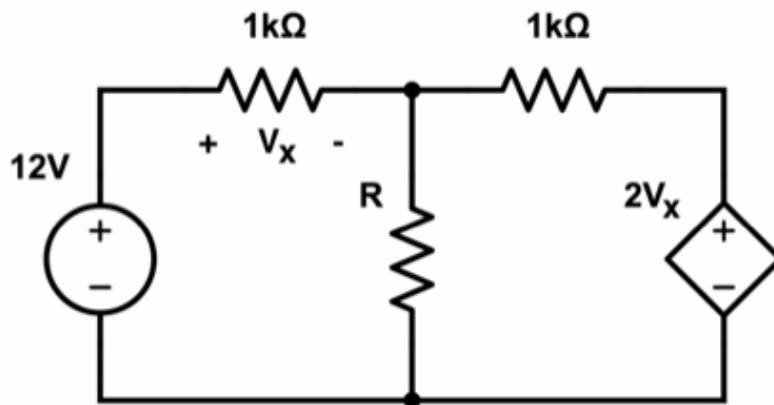Q. Find the value of R for which the power transferred across R is maximum. Calculate that maximum power transferred.



A. Calculating V_{TH} :

$$V_{TH} = 12 - 10^3 \cdot \frac{12}{4 \times 10^3} = 9V$$

Calculating I_{sc} :

$$I_{sc} = \frac{12}{10^3} - \left(\frac{-24}{10^3} \right) = 36 \text{ mA}$$


$$\Rightarrow R_{TH} = \frac{9V}{36 \text{ mA}} = 250 \Omega$$

R should be equal to $R_{TH} = 250 \Omega$ for maximum power transfer.

$$\text{Hence, } P_R = \left(\frac{9}{250 + 250} \right)^2 (250) = 81 \text{ mW}$$

Q. A linear network is connected to a variable resistor with an ideal voltmeter and ammeter as shown in the figure.

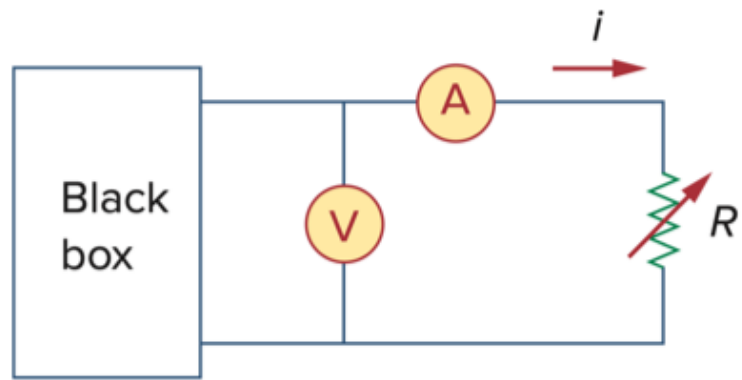Three readings were measured and tabulated as shown below.



$R(\Omega)$	$V(V)$	$i(A)$
2	6	3
8	16	2
14	21	1.5


Calculate the maximum power from the box.

A. Using Thevenin's equivalent,

We have,

$$V_{TH} - i Z_{TH} = V$$


$$V = iR$$

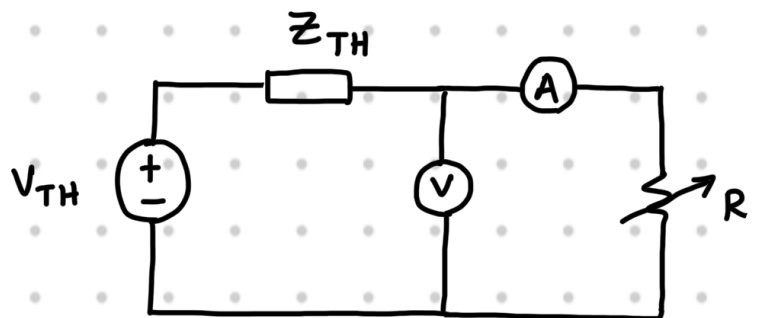

$$\Rightarrow \left. \begin{aligned} V_{TH} - 3 Z_{TH} &= 6 \\ V_{TH} - 2 Z_{TH} &= 16 \end{aligned} \right\} \begin{aligned} Z_{TH} &= 10 \Omega \\ V_{TH} &= 36 V \end{aligned}$$

$$\text{Hence, } P_{\max} = \frac{V_{TH}^2}{4 Z_{TH}} = 32.4 \text{ W}$$

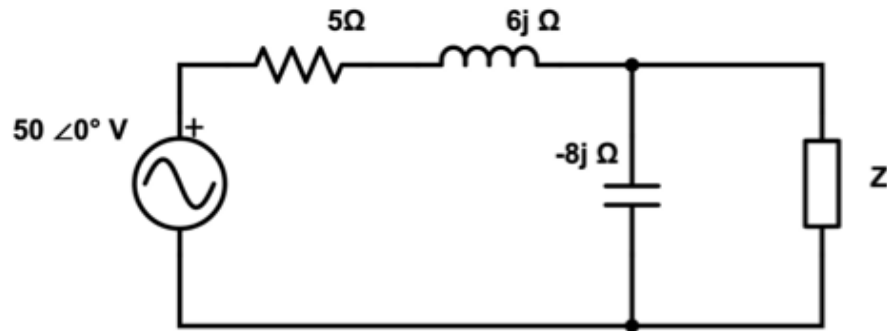Q. Find the value of Z for which the power transferred across Z is maximum. Calculate that maximum power transferred.



A. Calculating V_{TH} :

$$V_{TH} = \frac{50 \angle 0^\circ}{5 + 6j - 8j} (-8j) = \frac{400}{29} (2 - 5j) \approx 74.28 \angle -68.2^\circ$$

$$Z_{TH} = \frac{(5 + 6j)(-8j)}{(5 + 6j - 8j)} = \frac{320 - 104j}{29}$$

For maximum power transfer, $Z = Z_{TH}^*$

$$\Rightarrow Z = \frac{320 + 104j}{29}$$

Maximum power transferred :

$$P_Z = \frac{|V_{TH}|^2}{4 R_{TH}} = \frac{(74.28)^2}{4 \left(\frac{320}{29} \right)}$$

$$\Rightarrow P_Z = 125 \text{ W}$$