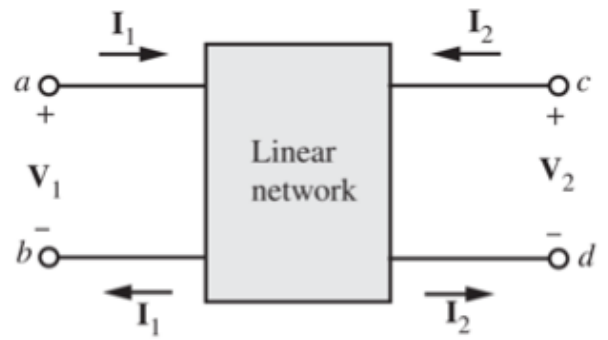


H / Hybrid Parameters

$$(V_1, I_2) = f(I_1, V_2)$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$



Hence, $V_1 = h_{11} I_1 + h_{12} V_2$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Hybrid parameters are very useful in the analysis of electronic circuits like modeling transistors.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}, \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

short-circuit
input impedance


open-circuit reverse
voltage gain

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}, \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$


short-circuit
forward current gain

open-circuit
output admittance

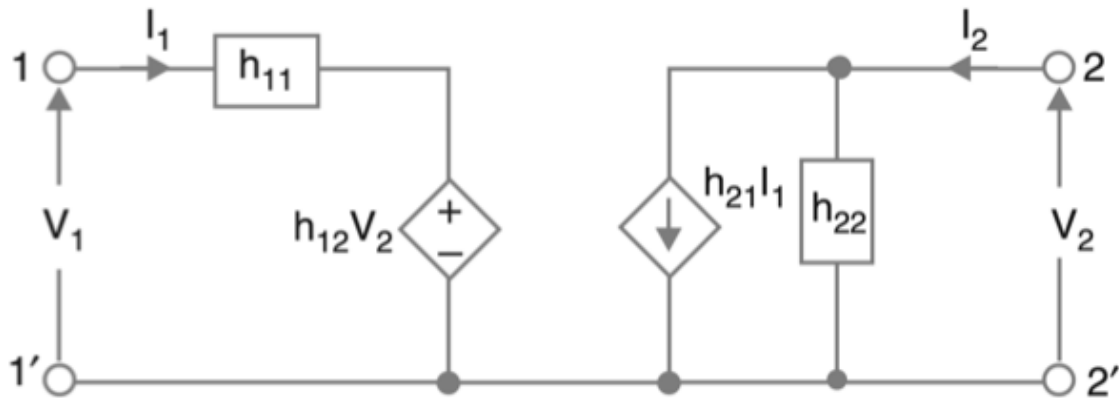The equivalent circuit representation is given in the figure below.



Condition for Reciprocity & Symmetry:

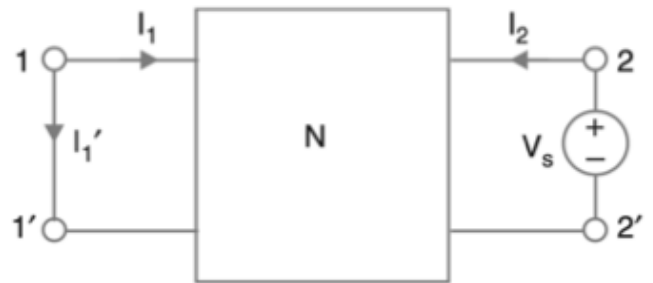

For reciprocity,

$$I_1' = I_2' \Rightarrow -V_s \frac{h_{21}}{h_{11}} = V_s \frac{h_{12}}{h_{11}}$$


$$\Rightarrow \underline{\underline{h_{21} = -h_{12}}}$$

For symmetry,

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\Rightarrow h_{11} h_{22} - h_{12} h_{21} = 1 \quad \text{or} \quad \begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1$$

Q. Determine the H-parameters of :

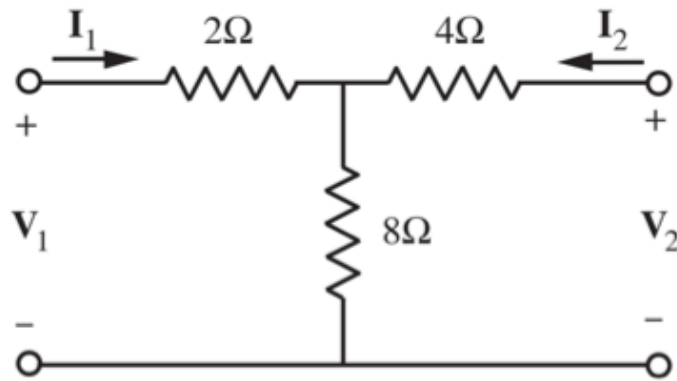

$$A. \begin{bmatrix} 10 & 8 \\ 8 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow V_1 = \frac{14}{3} I_1 + \frac{2}{3} V_2$$

$$\text{and } I_2 = -\frac{2}{3} I_1 + \frac{1}{12} V_2$$

Hence,


$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{14}{3} \Omega$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{2}{3}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -\frac{2}{3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{12} \Omega^{-1}$$

Q. Determine the H-parameters of :

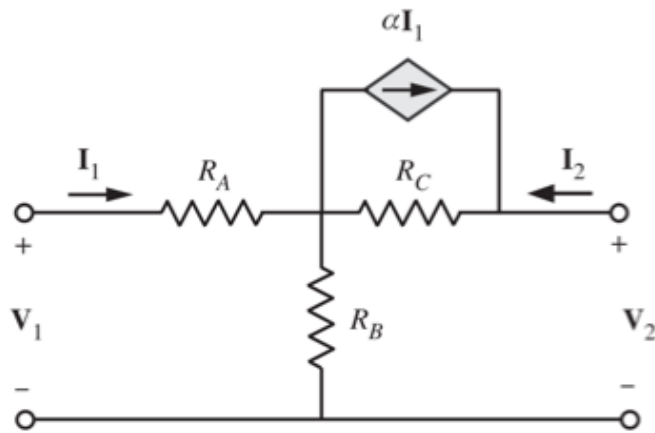

A. We have, $I_1(R_A + R_B) + I_2 R_B = V_1$

$$I_1(R_B + \alpha R_C) + I_2(R_B + R_C) = V_2$$

Hence,


$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{(R_A R_B + R_A R_C + R_B R_C - \alpha R_B R_C)}{(R_B + R_C)}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_B}{R_B + R_C}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -\frac{(R_B + \alpha R_C)}{R_B + R_C}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_B + R_C}$$

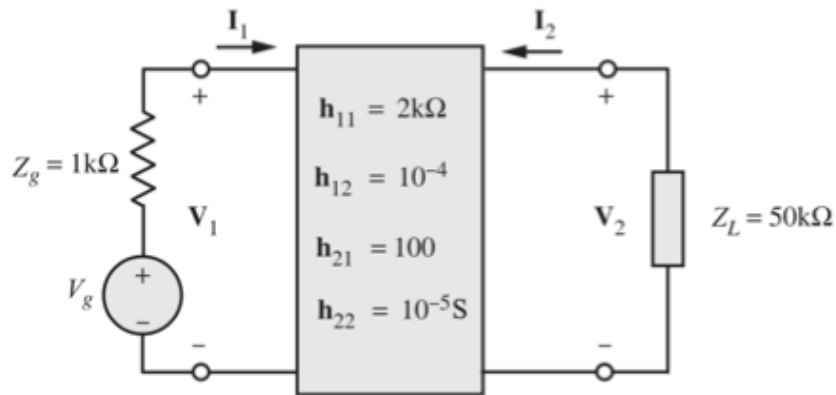Q. Determine $\frac{V_2}{V_g}$ of the circuit :



$$A. \quad V_1 = 2000 I_1 + 10^{-4} V_2$$

$$I_2 = 100 I_1 + 10^{-5} V_2$$

substituting $V_1 = V_g - 1000 I_1$

and $V_2 = -50 \cdot 10^3 I_2$


gives,

$$I_1 = \frac{3}{200} I_2$$

$$\Rightarrow V_g = 40 I_2$$

Hence, $\frac{V_2}{V_g} = -1250$

Q. Determine the input impedance of :

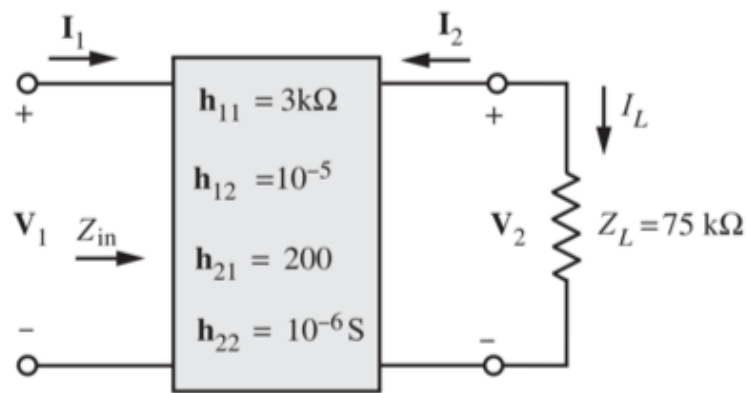

A. We have, $V_1 = 3 \times 10^3 I_1 + 10^{-5} V_2$

$$I_2 = 200 I_1 + 10^{-6} V_2$$

Also, $V_2 = -75 \times 10^3 I_2$


$$\Rightarrow I_2 = \frac{8000}{43} I_1$$

$$\Rightarrow V_2 = -\frac{60}{43} 10^7 I_1$$


$$\Rightarrow V_1 = 3000 I_1 - \frac{6000}{43} I_1 = \frac{123}{43} \cdot 10^3 I_1$$

Hence, $Z_{in} = \frac{V_1}{I_1} = \frac{123}{43} \cdot 10^3 \approx 2.86\text{ k}\Omega$

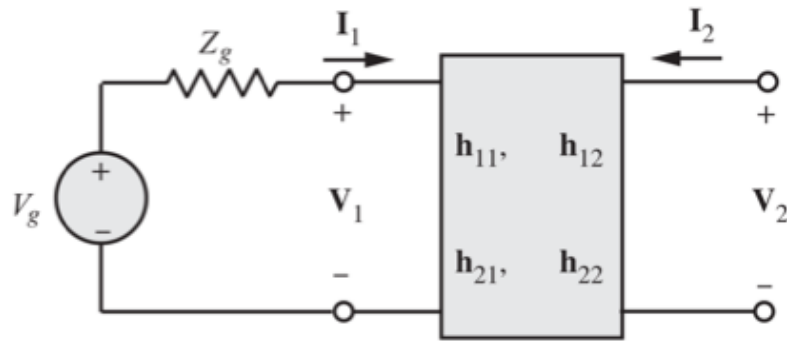Q. Determine the Thevenin equivalent circuit at the output of :



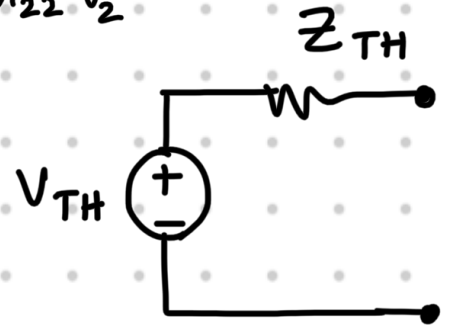A. We have , $V_1 = h_{11} I_1 + h_{12} V_2$
 $I_2 = h_{21} I_1 + h_{22} V_2$



To find V_{TH} : $I_2 = 0$

$$\Rightarrow V_{TH} = V_2 = \frac{-h_{21}}{h_{22}} I_1 = \frac{-h_{21}}{h_{22}} \left(\frac{V_g - h_{12} V_2}{Z_g + h_{11}} \right)$$

Hence, $V_{TH} = V_2 = \frac{-h_{21} V_g}{Z_g h_{22} + h_{11} h_{22} - h_{12} h_{21}}$

To find Z_{TH} : $V_1 = -I_1 Z_g$

$$\Rightarrow Z_{TH} = \frac{V_2}{I_2} = \frac{Z_g + h_{11}}{Z_g h_{22} + h_{11} h_{22} - h_{12} h_{21}}$$