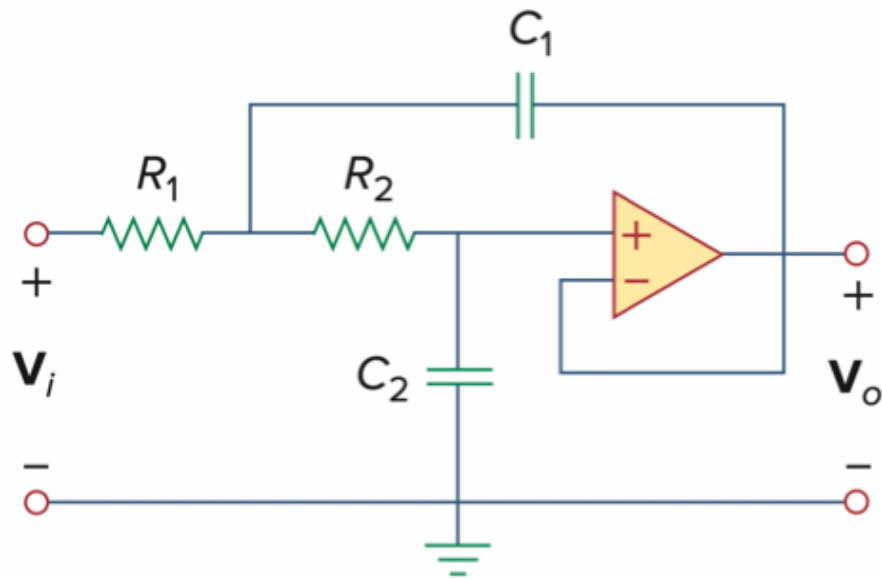


Q. What type of filter is shown below?




A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{R_1} \cdot \frac{1}{R_2}}{\frac{1}{R_1} \cdot \frac{1}{R_2} + sC_2 \left(\frac{1}{R_1} + \frac{1}{R_2} + sC_1 \right)}$$
$$\Rightarrow H(s) = \frac{1}{1 + sC_2(R_1 + R_2 + sR_1R_2C_1)}$$

$$H(0) = 1 \quad \text{and} \quad H(\infty) = 0$$

Hence, this is a low-pass filter.

Q. What type of filter is shown below?

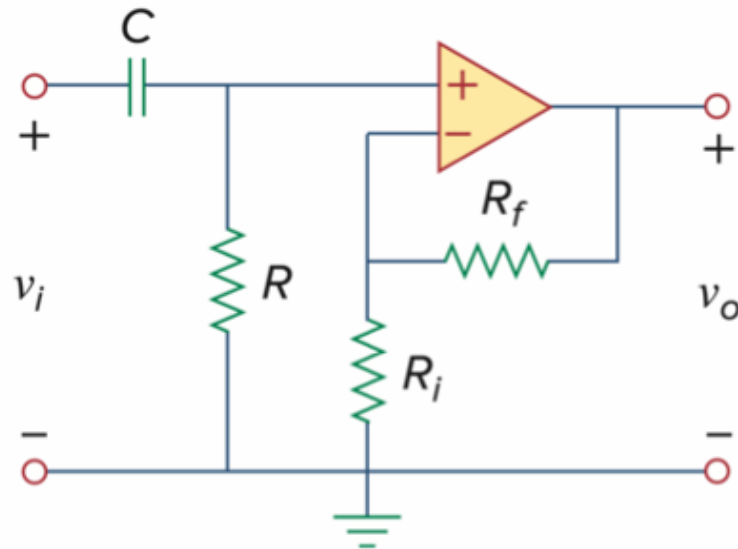

A. Solving the KCL/KVL equations,


$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{sRC}{1 + sRC}}{\frac{R_i}{R_i + R_f}}$$

$$\Rightarrow H(s) = \left(1 + \frac{R_f}{R_i}\right) \cdot \left(\frac{sRC}{1 + sRC}\right)$$

$$H(0) = 0 \quad \text{and} \quad H(\infty) = 1 + \frac{R_f}{R_i}$$

Hence, this is a high-pass filter.

Q. What type of filter is shown below?

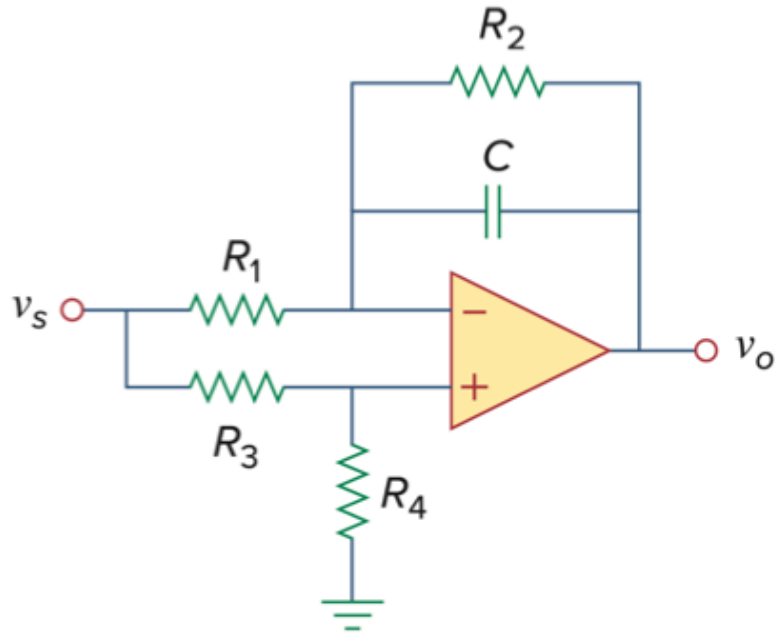

A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_4}{R_3 + R_4} \left(\frac{s + \frac{R_1 R_4 - R_2 R_3}{R_1 R_2 R_4 C}}{s + \frac{1}{R_2 C}} \right)$$

$$\Rightarrow H(s) = \frac{R_4}{R_3 + R_4} \frac{s + \frac{1}{R_1 C} \left(\frac{R_1}{R_2} - \frac{R_3}{R_4} \right)}{s + \frac{1}{R_2 C}}$$


This circuit can be used as both LPF & HPF.

For LPF : Choose $R_3 \rightarrow \infty \Rightarrow H(s) = \frac{-\frac{1}{R_1 C}}{s + \frac{1}{R_2 C}}$

For HPF :

Choose $R_1 R_4 = R_2 R_3 \Rightarrow H(s) = \frac{R_4}{R_3 + R_4} \cdot \frac{s}{s + \frac{1}{R_2 C}}$

Q. What type of filter is shown below?

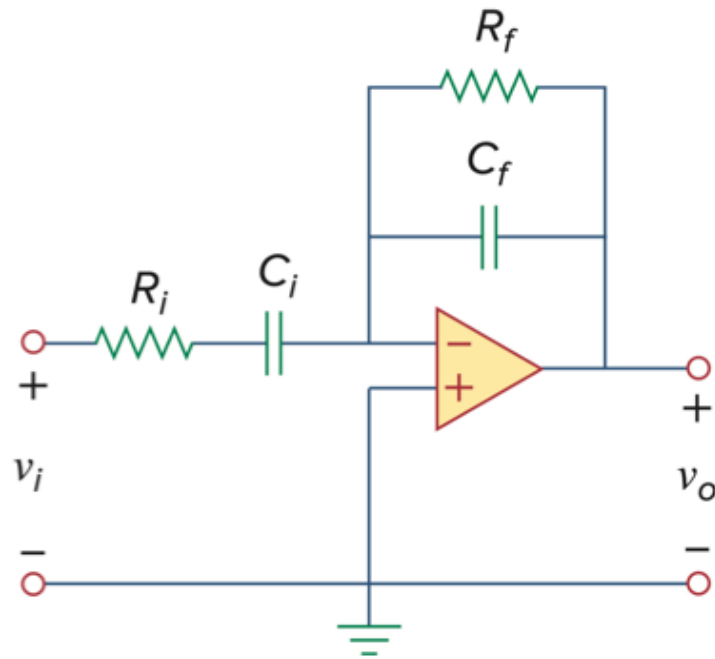

A. Solving the KCL/KVL equations,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{-R_f}{1 + s R_f C_f}}{\frac{1 + s R_i C_i}{s C_i}}$$

$$\Rightarrow H(s) = \frac{-R_f C_i s}{(1 + s R_f C_f)(1 + s R_i C_i)}$$

$$H(0) = H(\infty) = 0$$

Hence, this is a band-pass filter.