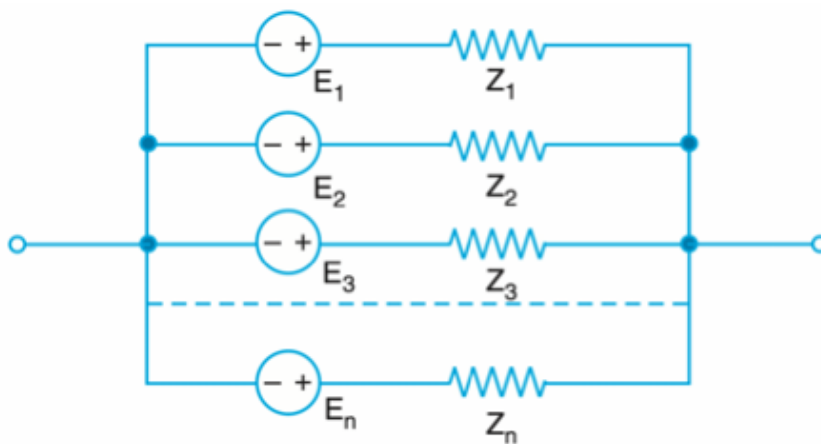


Millman's Theorem:

Part I: Any circuit containing multiple voltage sources, each one in series with its own resistance can be replaced by an equivalent voltage source in series with an equivalent resistance.

Let E_i ($i = 1, 2, \dots, n$) be the open-circuit voltages of n voltage sources having internal impedances Z_i in series, respectively, as shown in the figure.




Then, using Norton's theorem, we can have

$$I_i = \frac{E_i}{Z_i}$$


$$\text{and } Y_i = \frac{1}{Z_i}$$

$$i = 1, 2, \dots, n$$

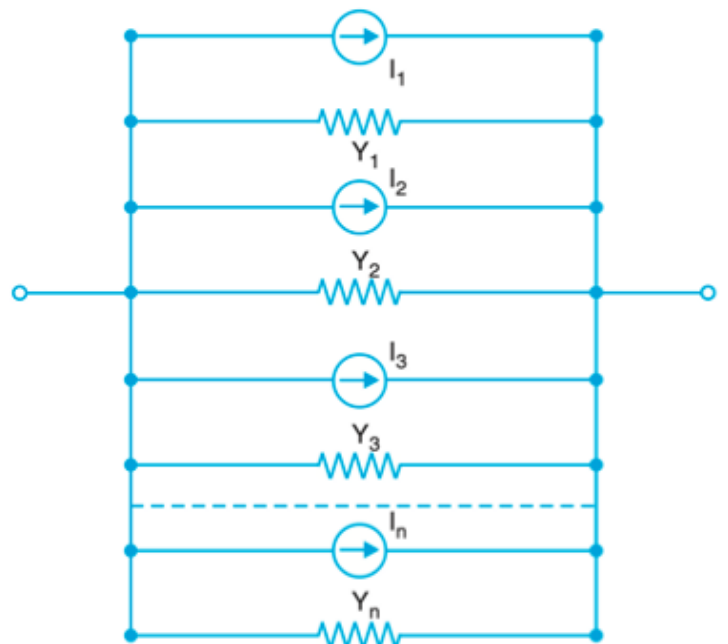

Next, summing up all the current sources and the admittances,

$$I = \sum_{i=1}^n I_i$$

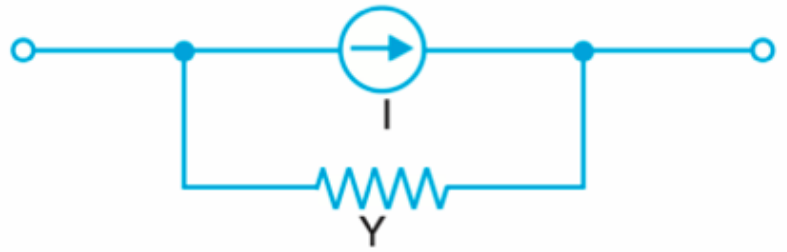

$$I = \frac{\sum_{i=1}^n E_i}{\sum_{i=1}^n Z_i} = \sum_{i=1}^n E_i \gamma_i$$

and
$$\gamma = \sum_{i=1}^n \gamma_i = \frac{1}{\sum_{i=1}^n Z_i}$$

Finally, we can write the Thevenin's equivalent of the circuit,




$$E = I Z$$

Hence,
$$E = \frac{I}{\gamma} = \frac{\sum_{i=1}^n E_i \gamma_i}{\sum_{i=1}^n \gamma_i}$$


and
$$Z = \frac{1}{\gamma} = \frac{1}{\sum_{i=1}^n \gamma_i}$$

Part II: Any circuit containing multiple current sources, each one in parallel with its own admittance can be replaced by an equivalent current source in parallel with an equivalent admittance.

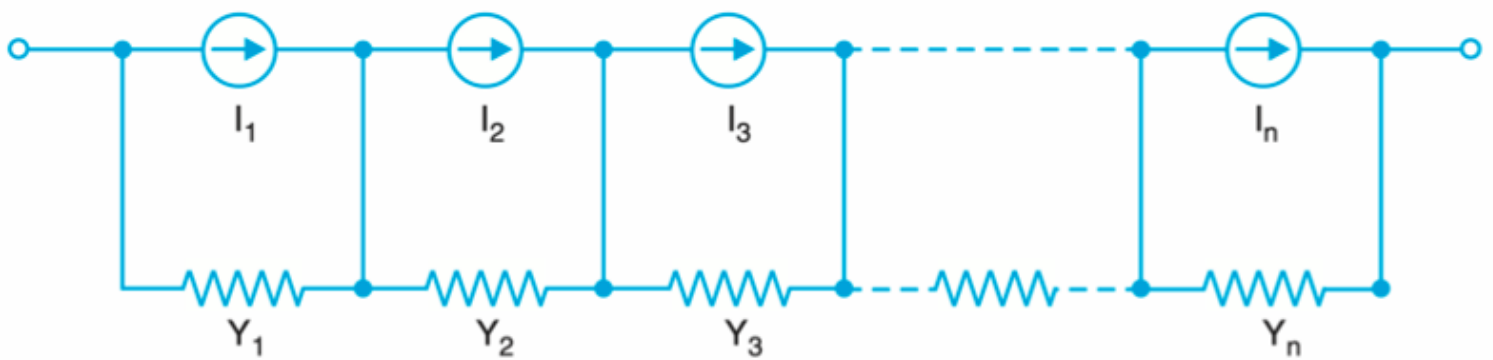Let I_i ($i = 1, 2, \dots, n$) be the n current sources having internal admittances Y_i in parallel as shown.



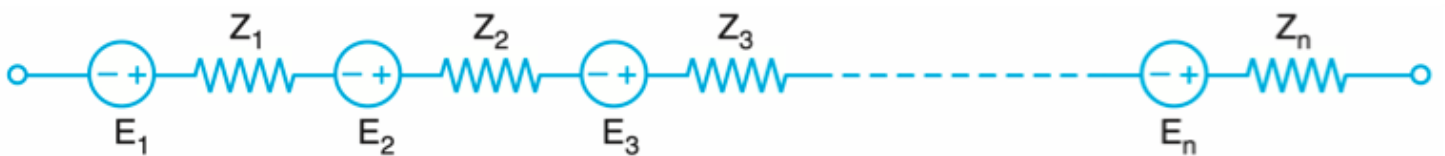Then, using Thevenin's theorem, we can have



$$E_i = \frac{I_i}{Y_i} \quad \text{and} \quad Z_i = \frac{1}{Y_i}$$

$$i = 1, 2, \dots, n$$

Next, summing up all the voltage sources and the impedances,


$$E = \sum_{i=1}^n E_i$$



$$E = \sum_{i=1}^n \frac{I_i}{Y_i} \quad \text{and} \quad Z = \sum_{i=1}^n Z_i = \sum_{i=1}^n \frac{1}{Y_i}$$

Finally, we can write the Norton's equivalent of the circuit,

$$I = \frac{E}{Z}$$

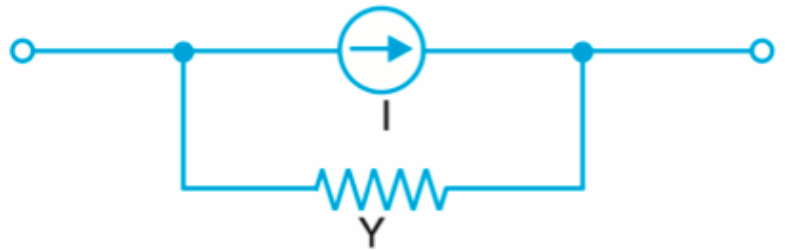


$$I = \frac{\sum_{i=1}^n \frac{I_i}{Y_i}}{\sum_{i=1}^n \frac{1}{Y_i}} \quad \text{and} \quad Y = \frac{1}{Z} = \frac{1}{\sum_{i=1}^n \frac{1}{Y_i}}$$

Note: Millman's theorem is an extension

of Thevenin's voltage equivalent and Norton's current-equivalent, taking a number of sources into account.

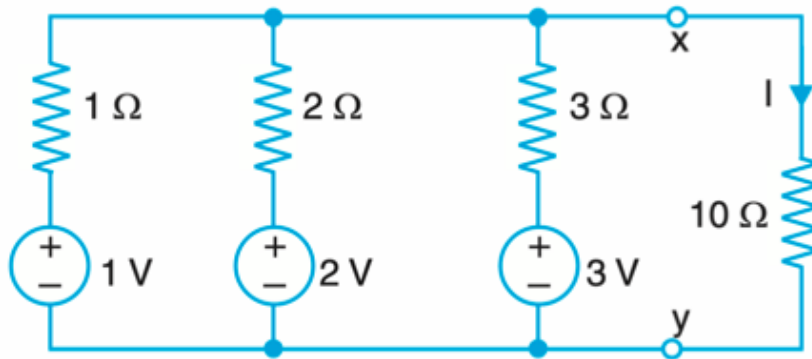
Q. Calculate the load current I in the circuit using Millman's theorem.



$$A. \quad Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{6}{11} \Omega$$


$$E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{3}{\frac{11}{6}} = \frac{18}{11} \text{ V}$$

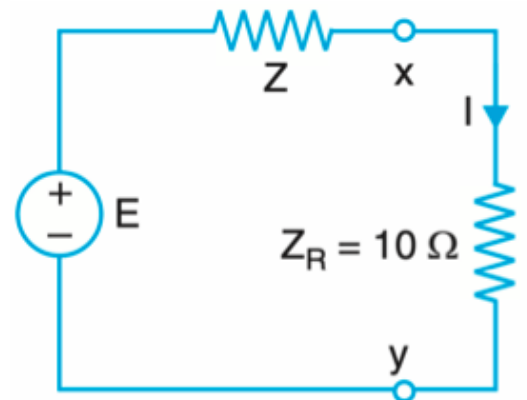Hence, from the Millman's equivalent circuit,



$$I = \frac{\frac{18}{11}}{\frac{6}{11} + 10} = \frac{9}{58} \text{ A}$$

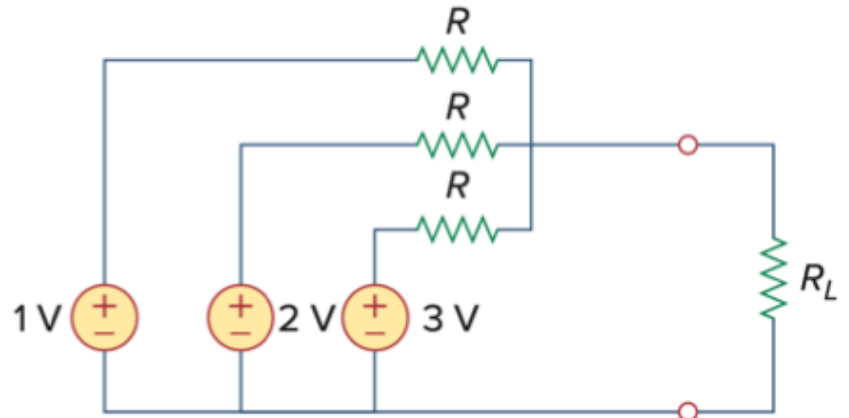Q. Determine the value of R such that the maximum power delivered to the load R_L is 12mW .



A. Using Millman's theorem,


$$Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{R}{3}$$

$$E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = 2V$$

$$P_{\max} = 12\text{mW}$$

$$\Rightarrow \frac{4}{4 \cdot \frac{R}{3}} = 12\text{mW}$$


$$\Rightarrow R = 250\Omega$$

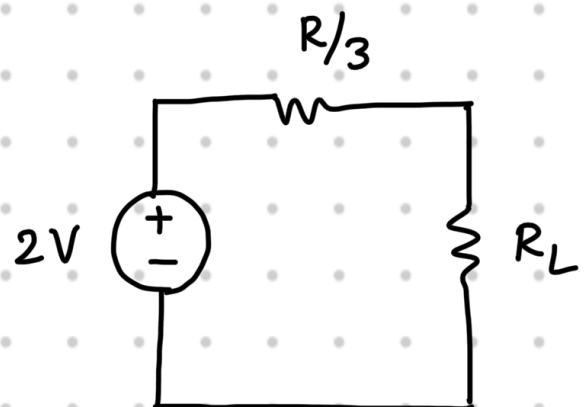

Q. Using Millman's Theorem,

determine the voltage

V_A of the network.

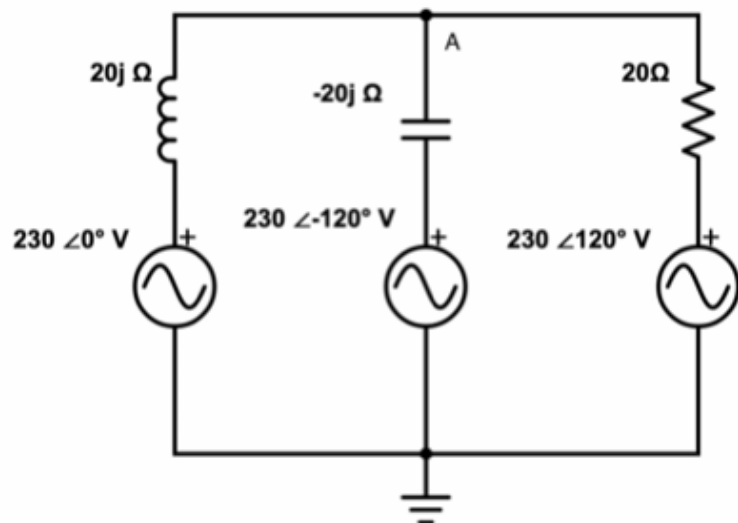


$$A. \quad Y = Y_1 + Y_2 + Y_3 = \frac{1}{20j} - \frac{1}{20j} + \frac{1}{20} = \frac{1}{20}$$

$$Z = \frac{1}{Y} = 20 \Omega$$


$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3} = \frac{-11.5j + 11.5 \angle -30^\circ + 11.5 \angle 120^\circ}{0.05}$$

$$\Rightarrow E = \frac{4.2 - 7.3j}{0.05} = 168.4 \angle -60^\circ \text{ V}$$

Hence, Millman's equivalent is:

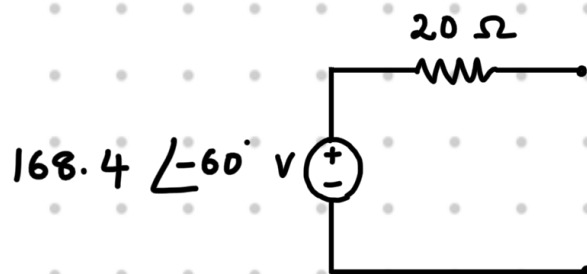

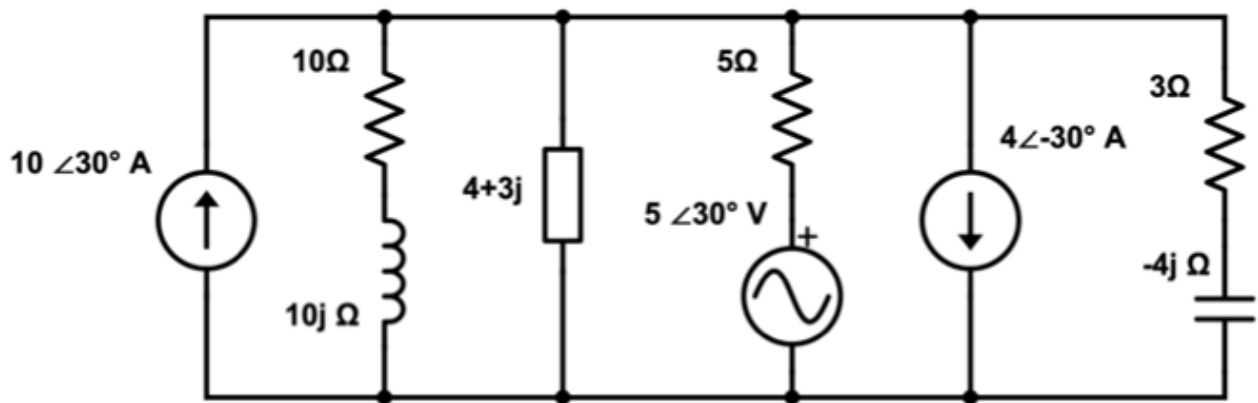Q. Using Millman's theorem, determine the current flowing through the impedance $4+3j$.




A. Replacing the current sources with voltage sources using source transformation,

$$Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{1}{\frac{1}{10+10j} + \frac{1}{5} + \frac{1}{3-14j}}$$

$$\Rightarrow Z = 2.6 \angle -16.56^\circ \Omega$$
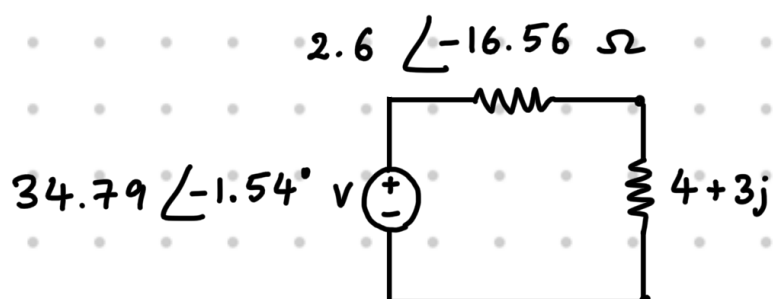
$$E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{13.432 \angle 15^\circ}{0.386 \angle 16.56^\circ} = 34.79 \angle -1.54^\circ$$



Hence,

$$I = 5.061 \angle -20.72^\circ \text{ A}$$