

Assignment - 2

EEEC201 - Signals, Systems, and Networks (Monsoon 2024)

Department of Electrical Engineering, IIT (ISM) Dhanbad

Due: 24.10.2024

1. Find the Laplace Transforms of the following:

(a) $(t + e^{-t} + t^2 e^{-t} + (t - 4)e^{2t})u(t)$ (b) $(\sin^2 t)u(t)$ (c) $\frac{\sin kt}{t}u(t)$

(d) $\cosh(t + \theta)u(t)$ (e) $(1 - (1 - t)e^{-3t})u(t)$ (f) $|t|e^{-|t|}$

(g) $x(t) = \begin{cases} t & 0 \leq t < 1 \\ e^t & t \geq 1 \\ 0 & \text{else} \end{cases}$ (h) $x(t) = \begin{cases} t - \pi & \pi \leq t < 2\pi \\ 0 & \text{else} \end{cases}$ (i) $(t \sin t)u(t)$

(j) $x(t) = \begin{cases} 1 & 0 \leq t < 2 \\ t^2 - 4t + 4 & t \geq 2 \\ 0 & \text{else} \end{cases}$ (k) $x(t) = \begin{cases} \cos(\pi t) & 0 < t < 4 \\ 0 & \text{else} \end{cases}$

Answer:

(a) $\frac{1}{s^2} + \frac{1}{s+1} + \frac{2}{(s+1)^3} + \frac{1}{(s-2)^2} - \frac{4}{s-2}$

(b) $\frac{2}{s(s^2 + 4)}$

(c) $\tan^{-1}\left(\frac{k}{s}\right)$

(d) $\frac{\sinh \theta + s \cosh \theta}{s^2 - 1}$

(e) $\frac{4s + 9}{s(s+3)^2}$

(f) $\frac{2(s^2 + 1)}{(s^2 - 1)^2}$

(g) $\frac{1}{s^2} + e^{-s}\left(\frac{e}{s-1} - \frac{1}{s} - \frac{1}{s^2}\right)$

(h) $\frac{e^{-\pi s}}{s^2} - e^{-2\pi s}\left(\frac{\pi}{s} + \frac{1}{s^2}\right)$

(i) $\frac{2s}{(s+1)^2}$

(j) $\frac{1}{s} + e^{-2s}\left(\frac{2}{s^3} - \frac{1}{s}\right)$

(k) $\frac{s(1 - e^{-4s})}{s^2 + \pi^2}$

2. Find the Inverse Laplace Transforms of the following:

$$\begin{array}{llll}
 \text{(a)} \quad \frac{24}{s^4} - \frac{9}{s^2 + 9} & \text{(b)} \quad \frac{8}{s^3 + 4s} & \text{(c)} \quad \frac{1 + e^{-2s}}{s^2 + 6} & \text{(d)} \quad \frac{2s + 3}{s^2 + 4s + 13} \\
 \text{(e)} \quad \frac{1}{(s + 1)(s^2 - 1)} & \text{(f)} \quad \frac{s^2 - 2s}{s^4 + 5s^2 + 4} & \text{(g)} \quad \frac{e^{-3s}}{s - 2} & \text{(h)} \quad \frac{5(s + 2)^2}{s(s + 1)^3} \\
 \text{(i)} \quad \frac{2s + 5}{s^2 + 5s + 6} e^{-2s} & \text{(j)} \quad \frac{s}{(s - 3)^5} & \text{(k)} \quad \frac{3 + e^{-(s-1)}}{s^2 - 2s + 5} & \text{(l)} \quad \frac{9 + s}{4 - s^2}
 \end{array}$$

Answer:

$$\begin{array}{ll}
 \text{(a)} \quad (4t^3 - 3 \sin(3t))u(t) \\
 \text{(b)} \quad (2 - 2 \cos(2t))u(t) \\
 \text{(c)} \quad \frac{\sin \sqrt{6}t}{\sqrt{6}}u(t) + \frac{\sin(\sqrt{6}(t - 2))}{\sqrt{6}}u(t - 2) \\
 \text{(d)} \quad \left(2 \cos 3t - \frac{\sin 3t}{3} \right) e^{-2t}u(t) \\
 \text{(e)} \quad \frac{e^t - 2te^{-t} - e^{-t}}{4}u(t) \\
 \text{(f)} \quad \frac{2 \cos 2t + 2 \sin 2t - 2 \cos t - \sin t}{3}u(t) \\
 \text{(g)} \quad e^{2(t-3)}u(t - 3) \\
 \text{(h)} \quad \left(20 - e^{-t}(2.5t^2 + 15t + 20) \right)u(t) \\
 \text{(i)} \quad (e^{-2(t-2)} + e^{-3(t-2)})u(t - 2) \\
 \text{(j)} \quad e^{3t} \left(\frac{t^3}{6} + \frac{t^4}{8} \right)u(t) \\
 \text{(k)} \quad \frac{3e^t}{2}(\sin 2t)u(t) + \frac{e^t}{2}(\sin 2(t - 1))u(t - 1) \\
 \text{(l)} \quad -(\cosh 2t + 4.5 \sinh 2t)
 \end{array}$$

3. Verify the Initial value theorem and the Final value theorem for the following:

$$\begin{array}{ll}
 \text{(a)} \quad e^{-t}(t + 2)^2 u(t) & \text{(b)} \quad (1 + e^{-t}(\sin t + \cos t)) u(t) \\
 \text{(c)} \quad t^2 e^{-3t} u(t) & \text{(d)} \quad u(t - T)
 \end{array}$$

Answer:

$$\begin{array}{ll}
 \text{(a)} \quad x(0^+) = 4, x(\infty) = 0 \\
 \text{(b)} \quad x(0^+) = 2, x(\infty) = 1 \\
 \text{(c)} \quad x(0^+) = 0, x(\infty) = 0 \\
 \text{(d)} \quad \text{If } T > 0: x(0^+) = 0, x(\infty) = 1 \\
 \quad \quad \text{If } T < 0: x(0^+) = 1, x(\infty) = 1
 \end{array}$$

4. Solve the following differential equations:


- (a) $y' + 3y = t^2 e^{-3t} + t e^{-2t} + t$ with $y(0) = 1$
- (b) $y'' + 4y = 0$ with $y(0) = 1, y'(0) = 6$
- (c) $y'' + 4y' + 8y = e^{-t}$ with $y(0) = y'(0) = 0$
- (d) $y''' - y' = 2$ with $y(0) = y'(0) = y''(0) = 4$
- (e) $y'' + 2y' + 5y = 0$ with $y(0) = 2, y'(0) = 0$
- (f) $y'' + 4y' + 3y = 10\cos(t)$ with $y(0) = 1, y'(0) = 2$
- (g) $y'' + 4y' + 4y = 3t e^{-2t}$ with $y(0) = 0, y'(0) = 1$
- (h) $y'''' + y = 0$ with $y(0) = y'(0) = y''(0) = y'''(0) = 1$

Answer:


- (a) $y(t) = \left(e^{-3t} \left(2 + \frac{t^3}{3} \right) + e^{-2t} (t - 2) + \frac{t}{3} - \frac{1}{9} \right) u(t)$
- (b) $y(t) = \cos 2t + 3 \sin 2t$
- (c) $\frac{2e^{-t} - e^{-2t}(2 \cos 2t + \sin 2t)}{10}$
- (d) $y(t) = 5e^t - e^{-t} - 2t$
- (e) $y(t) = e^{-t}(2 \cos 2t + \sin 2t)$
- (f) $y(t) = \cos t + 2 \sin t$
- (g) $y(t) = e^{-2t} \left(t + \frac{t^3}{2} \right)$
- (h) $y(t) = \frac{1}{\sqrt{2}} \left(\sin \left(\frac{t}{\sqrt{2}} \right) \cosh \left(\frac{t}{\sqrt{2}} \right) - \cos \left(\frac{t}{\sqrt{2}} \right) \sinh \left(\frac{t}{\sqrt{2}} \right) \right)$

5. Using KCL/KVL and Nodal/Mesh Analysis, answer the following:

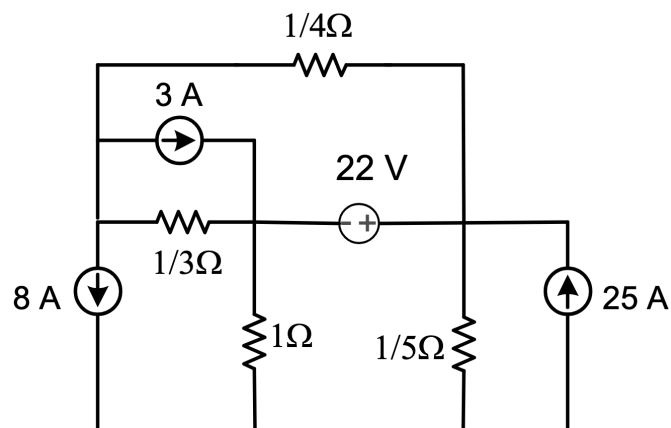
- (a) What are the node voltages in this circuit?



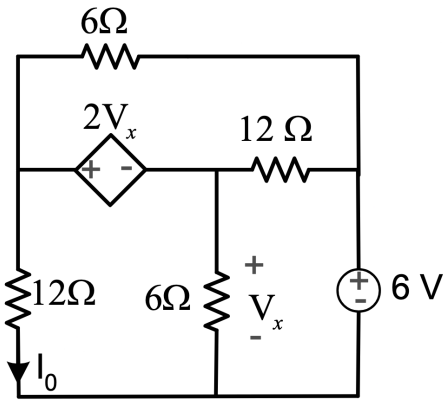
(b) Calculate the node voltages and the current I_0 in the circuit below.



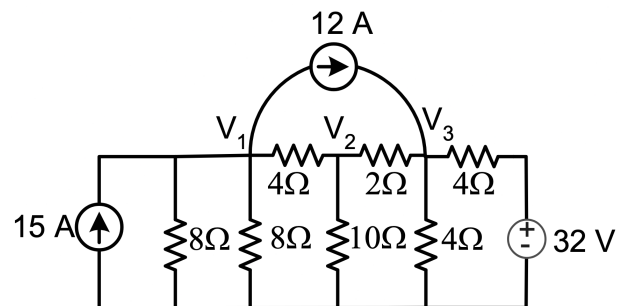
(c) What is the power dissipated by the 10 Ohm resistor?



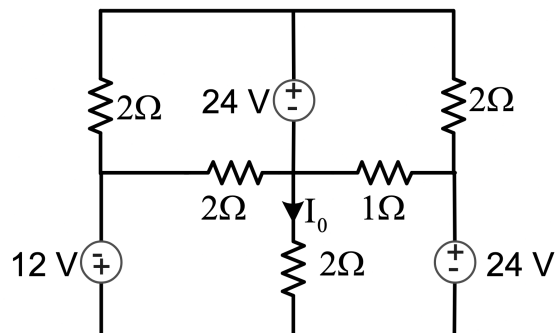
(d) What is the current I_0 in the circuit below?



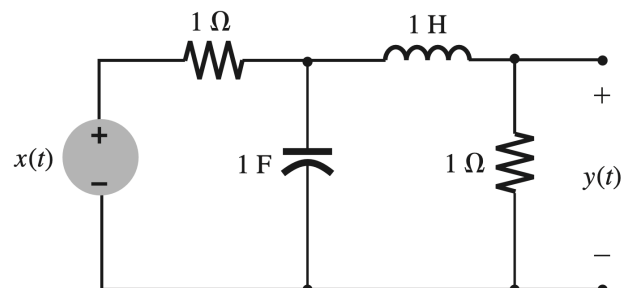
(e) If $x(t) = te^{-t}u(t)$ V, calculate $y(t)$:



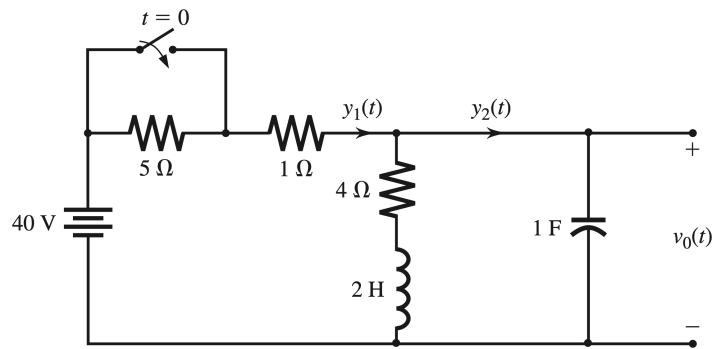
(f) If the switch is open for a long time and suddenly closed at $t = 0$, calculate $y_1(t)$ and $y_2(t)$:



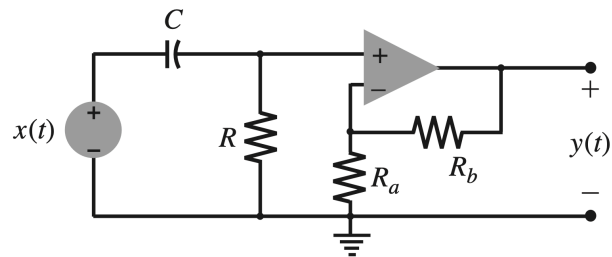
(g) What is the transfer function of this circuit?



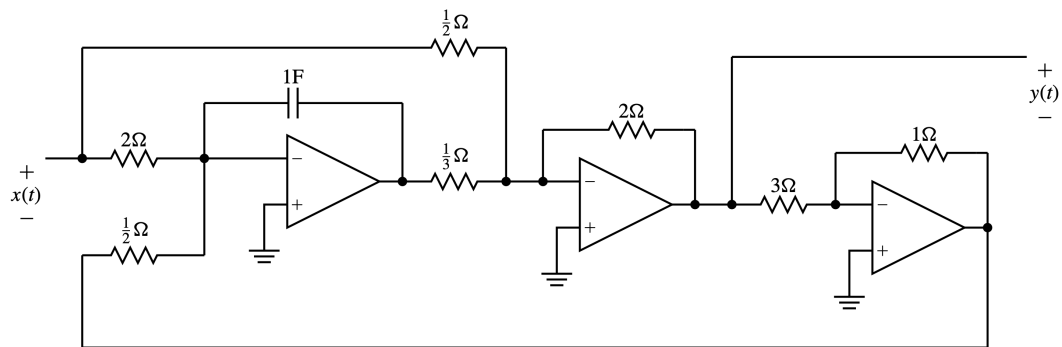(h) What is the transfer function of this circuit?




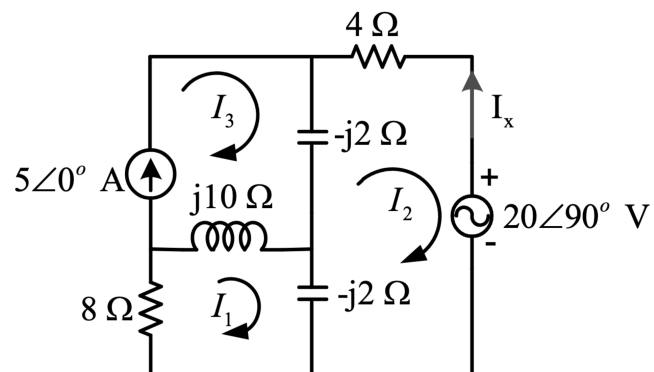(i) What is the current I_x flowing out of the voltage source?




(j) What is the voltage $V_0(t)$ across the capacitor?

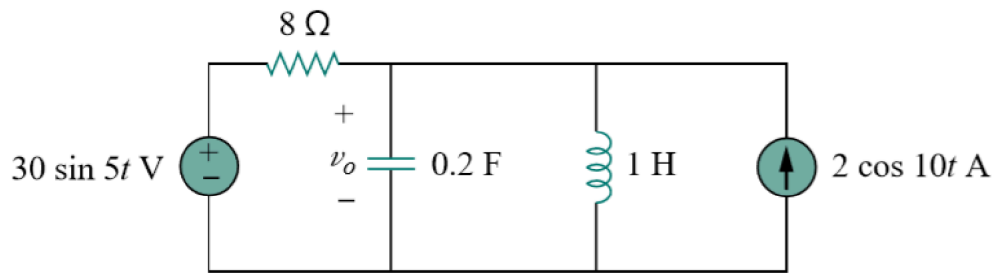
(Hint: Convert the circuit to phasor domain, solve the equations and then convert back to time domain.)



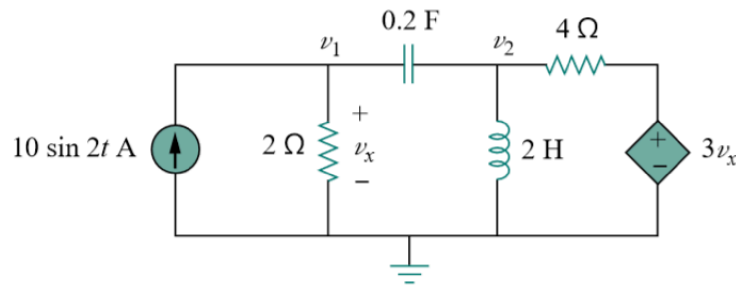(k) What are the node voltages v_1 and v_2 ?




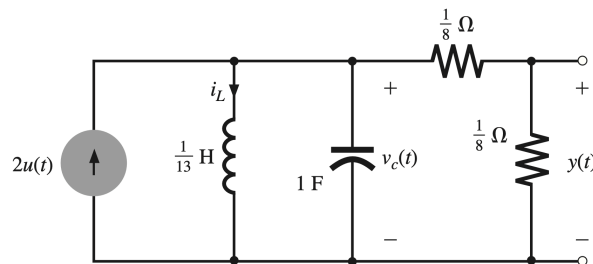(l) If $i_L(0^-) = 1A$ and $v_C(0^-) = 3V$, calculate the voltage $y(t)$ for $t \geq 0$.




(m) Assuming zero initial conditions and $\omega_0^2 = \frac{1}{LC}$, calculate the current $y(t)$ if

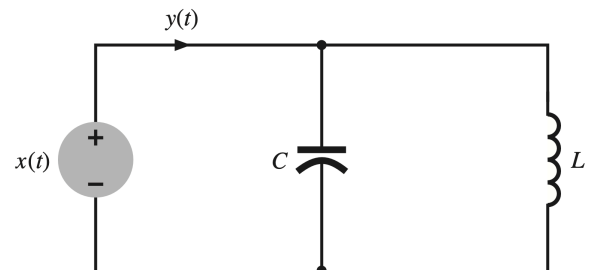
$$x(t) = (A \sin \omega_0 t + B \cos \omega_0 t)u(t)$$



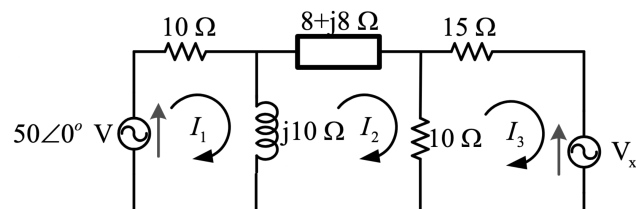
(n) What should be the value of V_x so that no current flows through the impedance $8 + 8j$?



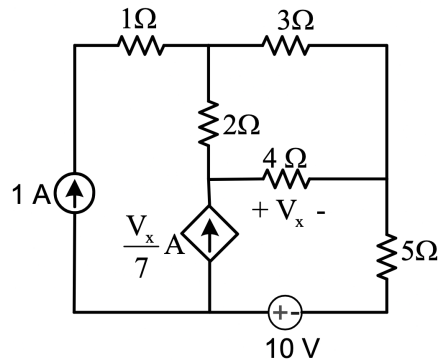
(o) What is the power dissipated or supplied by the voltage source?



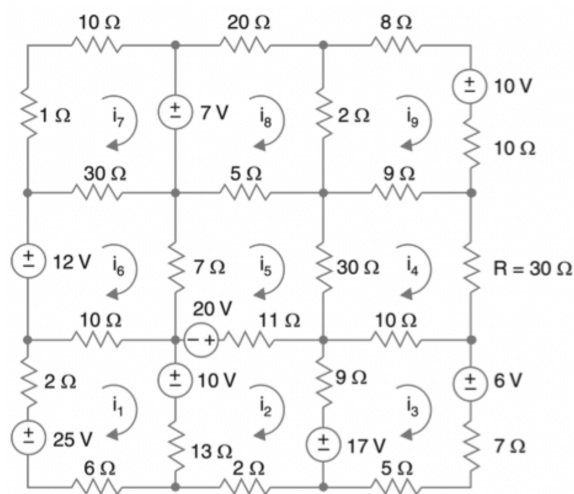
(p) What is the power dissipated by the 30 Ohm resistor?



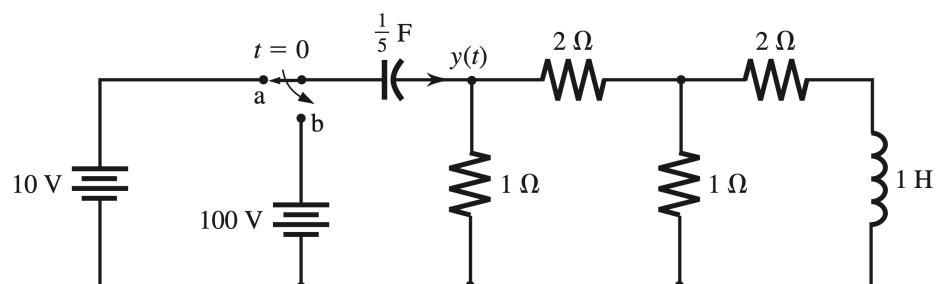
(q) If the switch is at “a” for a long time and suddenly moved to “b” at $t = 0$, calculate $y(t)$:



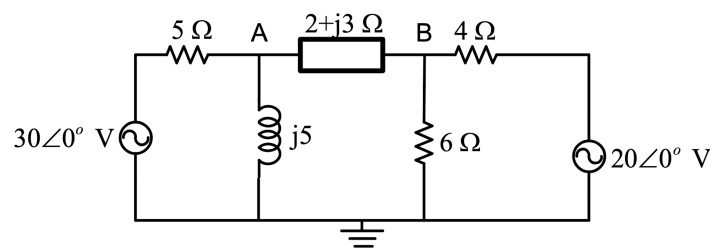
(r) What is the current flowing through the 6 Ohm resistor?



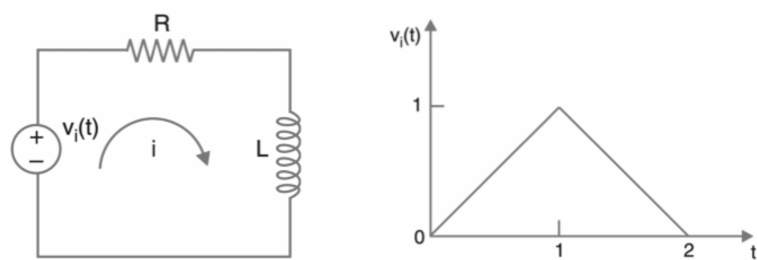
(s) Assuming zero initial conditions and $R = 2$ and $L = 2$, calculate the current in the circuit:



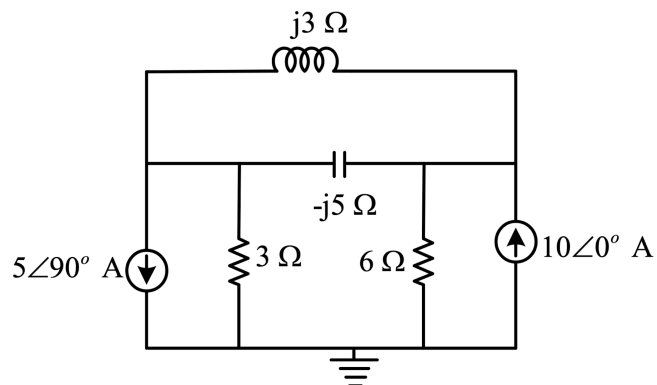
(t) What is the voltage across the 6 Ohm resistor?



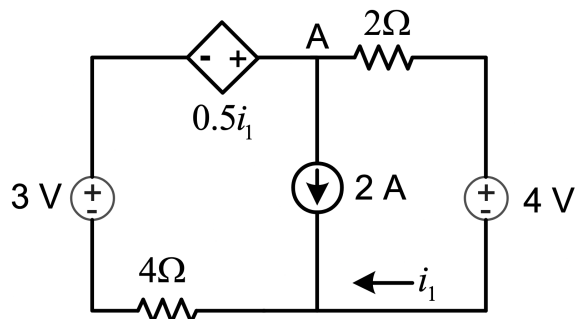
(u) Calculate the current flowing through the 4 Ohm resistor:



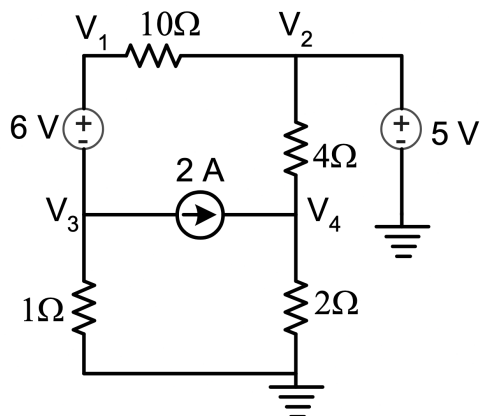(v) Calculate all the node voltages in the circuit below:



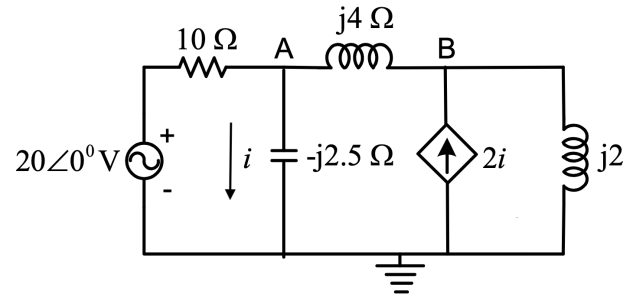(w) Calculate the current i in the circuit below:



Answer:

(a) $V_1 = -4.5V$, $V_2 = -15.5V$, $V_3 = 6.5V$

(b) $V_1 = 4.5V$, $V_2 = 1.5V$, $V_3 = 6V$, $I_0 = 0.375A$

(c) $P = 58.6 \text{ W}$

(d) $I_0 = 0 \text{ A}$

(e) $(te^{-t} - e^{-t} \sin t)u(t) \text{ V}$

(f) $y_1(t) = (8 + 17.9e^{-1.5t} \cos(0.5t - 26.56))u(t) \text{ A}$

$y_2(t) = 28.28e^{-1.5t} \cos(0.5t - 45))u(t) \text{ A}$

(g) $H(s) = \frac{s}{s+a} \left(1 + \frac{R_b}{R_a}\right)$

(h) $H(s) = \frac{3-4s}{4+s}$

(i) $I_x = 6.12 \angle 144.78^\circ \text{ A}$

(j) $V_0(t) = 4.63 \sin(5t - 81.12) + 1.05 \cos(10t - 86.24) \text{ V}$

(k) $v_1(t) = 20.96 \sin(2t + 58) \text{ V}$

$v_2(t) = 44.11 \sin(2t + 41) \text{ V}$

(l) $y(t) = 1.72e^{-2t} \cos(3t + 29))u(t) \text{ V}$

(m) $y(t) = \frac{A}{L\omega_0}u(t) + \frac{B}{L\omega_0^2}\delta(t)$

(n) $V_x = 88.4 \angle 45^\circ \text{ V}$

(o) $P = 48.66 \text{ W}$

(p) $P = 0.01 \text{ W}$

(q) $(121.6e^{-6.5t} - 1.6e^{-2.8t})u(t)$

(r) $I = 2.64 \angle 10^\circ \text{ A}$

(s) $i(t) = \left(\frac{t-1+e^{-t}}{2}\right)(u(t) - 2u(t-1) + u(t-2)) \text{ A}$

(t) $V = 34.4 \angle 24^\circ \text{ V}$

(u) $I = 2 - 1.636 = 0.364 \text{ A}$

(v) $V_1 = 4.37V$, $V_2 = 5V$, $V_3 = -1.63V$, $V_4 = 4.33V$

(w) $I = 0.8 \angle 92^\circ \text{ A}$

