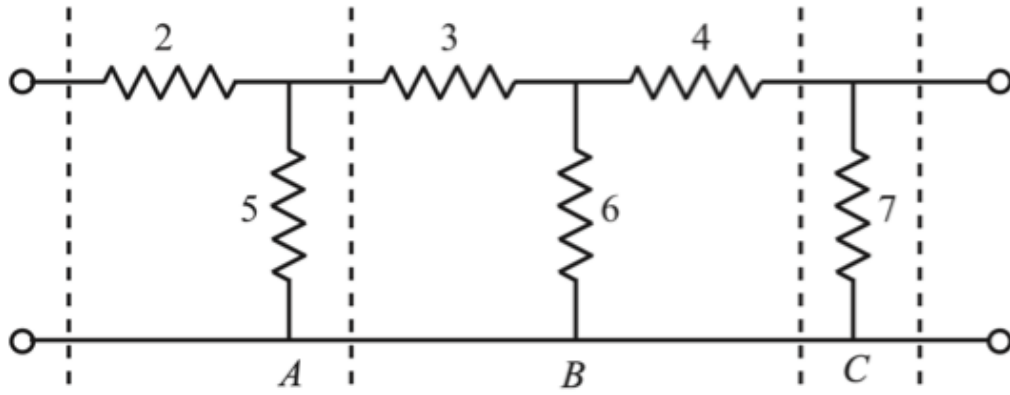


Q. Determine the ABCD-parameters of :



A. This is a cascade of three networks:

For the first network, $\begin{bmatrix} 7/5 & 2 \\ 1/5 & 1 \end{bmatrix}$
the ABCD-parameters are :


Similarly, for the second and third :

$$\begin{bmatrix} 3/2 & 9 \\ 1/6 & 5/3 \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} 1 & 0 \\ 1/7 & 1 \end{bmatrix}$$

The overall ABCD parameters of the cascade is the product of three matrices :

$$\begin{bmatrix} 7/5 & 2 \\ 1/5 & 1 \end{bmatrix} \begin{bmatrix} 3/2 & 9 \\ 1/6 & 5/3 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/7 & 1 \end{bmatrix} = \begin{bmatrix} \frac{989}{210} & \frac{239}{15} \\ \frac{101}{105} & \frac{52}{15} \end{bmatrix}$$

Q. Find $\frac{V_2}{V_s}$:

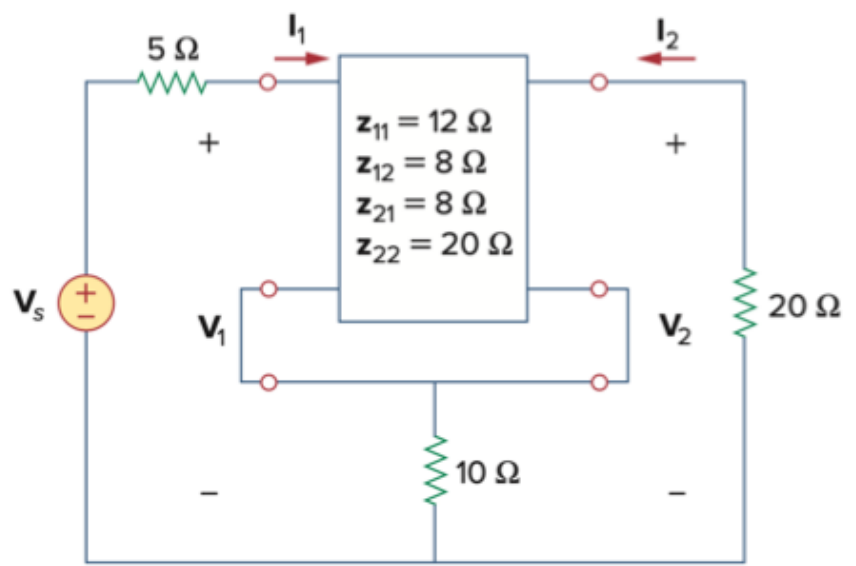

A. The two networks are in series.

$$\text{Hence, } [Z] = \begin{bmatrix} 12 & 8 \\ 8 & 20 \end{bmatrix} + \begin{bmatrix} 10 & 10 \\ 10 & 10 \end{bmatrix} = \begin{bmatrix} 22 & 18 \\ 18 & 30 \end{bmatrix}$$

$$\Rightarrow \begin{aligned} V_1 &= 22 I_1 + 18 I_2 \\ V_2 &= 18 I_1 + 30 I_2 \end{aligned}$$


Substituting $V_1 = V_s - 5 I_1$ and $V_2 = -20 I_2$

$$\Rightarrow I_2 = \frac{5}{36} V_2$$

$$\Rightarrow V_s = \frac{57}{20} V_2$$

$$\text{Hence, } \frac{V_2}{V_s} = \frac{20}{57}$$

Q. Find $\frac{V_o}{V_s}$:

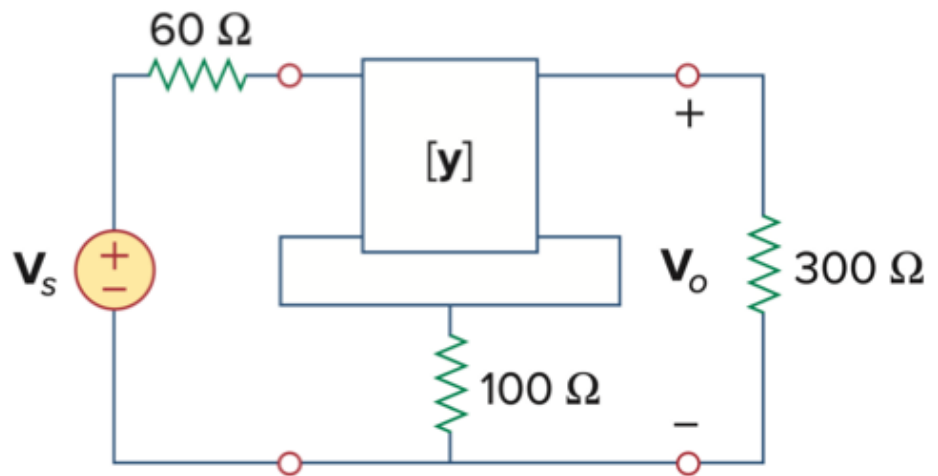

$$\text{Given } [y] = \begin{bmatrix} 0.002 & 0 \\ 0 & 0.01 \end{bmatrix} \Omega^{-1}.$$

A. These two-port networks are in series.

Hence, let us calculate z -parameters first.

$$[z] = \begin{bmatrix} 500 & 0 \\ 0 & 100 \end{bmatrix} + \begin{bmatrix} 100 & 100 \\ 100 & 100 \end{bmatrix}$$


$$\Rightarrow [z] = \begin{bmatrix} 600 & 100 \\ 100 & 200 \end{bmatrix}$$

$$\text{Hence, } V_s - 60 I_1 = 600 I_1 + 100 I_2$$

$$V_o = -300 I_2 = 100 I_1 + 200 I_2$$


$$\Rightarrow \frac{V_o}{V_s} = \frac{3}{32} = 0.09375$$

Q. Calculate the Y -parameters of :

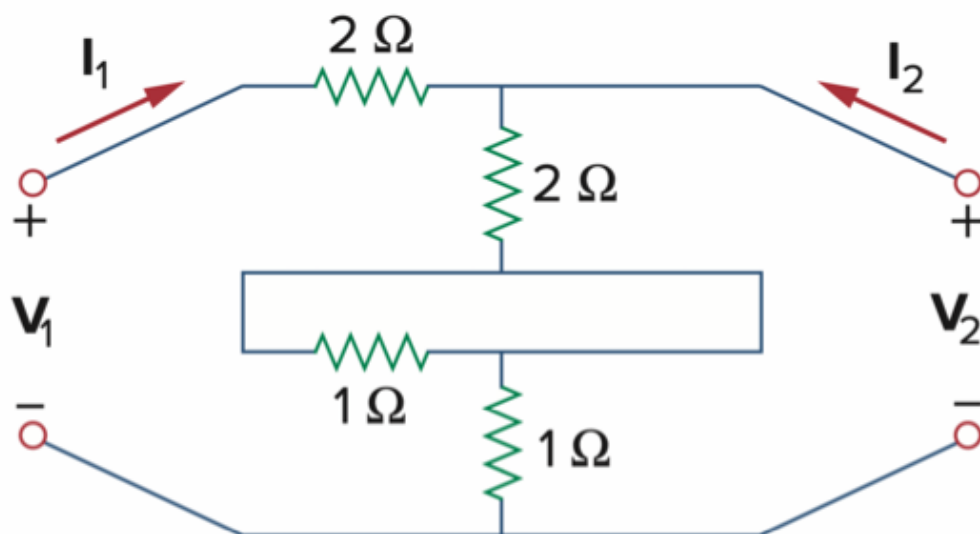

A. These two-port networks are in series.
Hence, let us calculate Z -parameters first.

However, note that 1Ω is shorted.

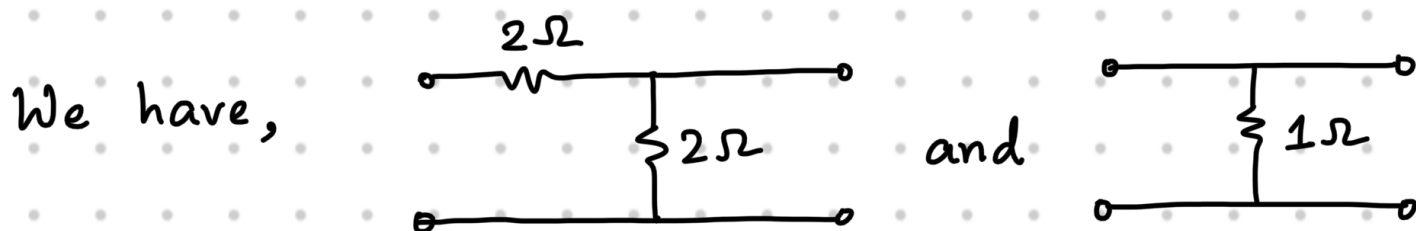


$$\Rightarrow [Z] = \begin{bmatrix} 4 & 2 \\ 2 & 2 \end{bmatrix} + \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} 5 & 3 \\ 3 & 3 \end{bmatrix}$$

Converting them into Y parameters:

$$[Y] = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix} = \begin{bmatrix} 1/2 & -1/2 \\ -1/2 & 5/6 \end{bmatrix} \Omega^{-1}$$

Q. Find the admittance parameters of:

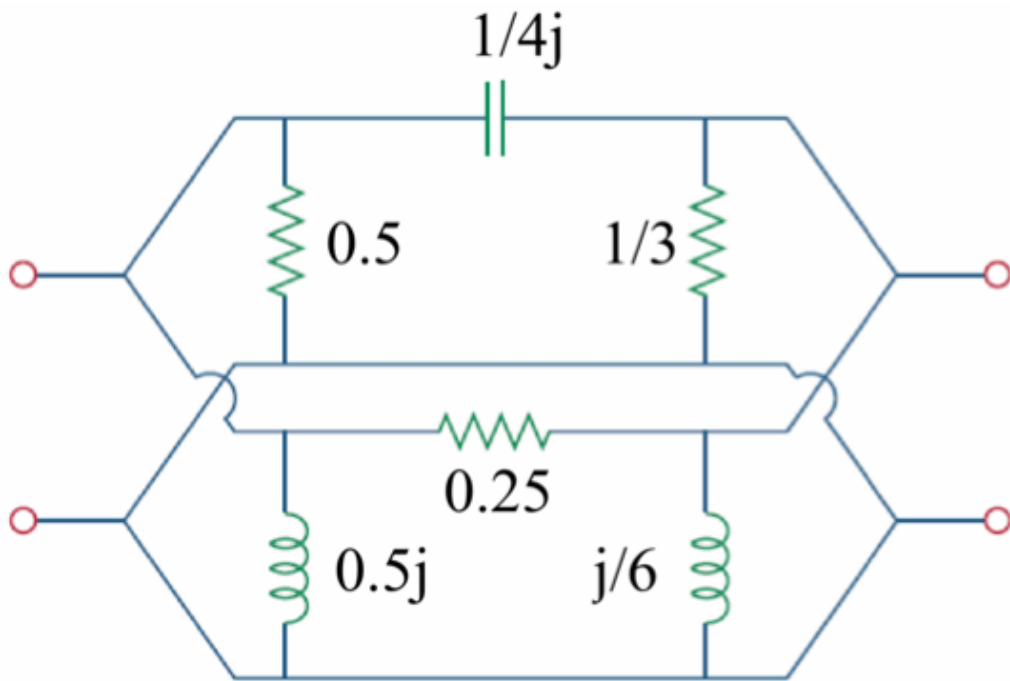

A.
$$[y_a] = \begin{bmatrix} 2 + 4j & -4j \\ -4j & 3 + 4j \end{bmatrix}$$

$$[y_b] = \begin{bmatrix} 4 - 2j & -4 \\ -4 & 4 - 6j \end{bmatrix}$$

Hence,
$$[y] = \begin{bmatrix} 6 + 2j & -4 - 4j \\ -4 - 4j & 7 - 2j \end{bmatrix}$$