


Compensation Theorem :

In a linear network N , if the current in a branch is I and the impedance Z of the branch is changed by δZ , then the incremental voltage and current in each branch of the network is that voltage or current that would be produced by an opposing voltage source of value $V_c = I \delta Z$ introduced in the altered branch after the modification.

Consider the circuit shown below:


We have,

$$I = \frac{V_{oc}}{Z + Z_{th}}$$

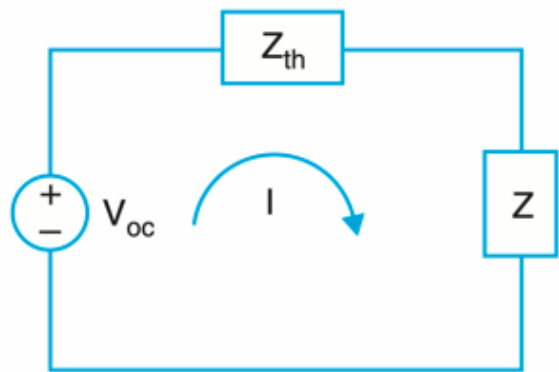

Let δZ be the change in Z , Then
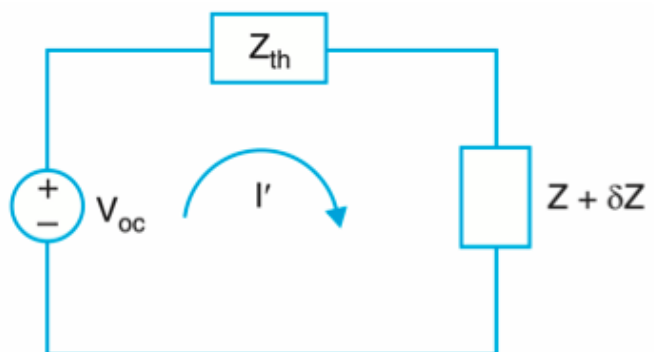
$$I' = \frac{V_{oc}}{Z + \delta Z + Z_{th}}$$




$$\Rightarrow \delta I = I' - I = \frac{V_{oc}}{Z + \delta Z + Z_{th}} - \frac{V_{oc}}{Z + Z_{th}}$$

$$\Rightarrow \delta I = \frac{-V_{oc}}{Z + Z_{th}} \cdot \frac{\delta Z}{Z + \delta Z + Z_{th}}$$

$$= \frac{-I \delta Z}{Z + \delta Z + Z_{th}} = \frac{-V_c}{Z + \delta Z + Z_{th}}$$


$$\text{where } V_c = I \delta Z$$

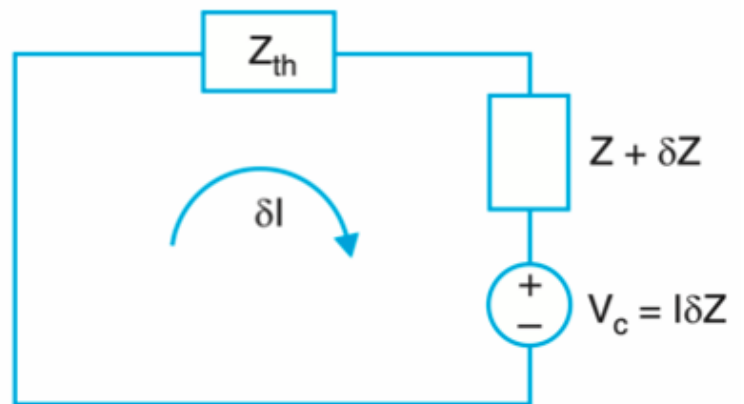Hence, this shows that the change in current δI due to a change in any branch in a linear network can be calculated



by determining the current in that branch in a network obtained from the original network by nulling all the independent sources and placing a voltage source called the compensation source in series with the branch whose value is $V_c = I \delta Z$ as shown above. Note that the direction of V_c is opposite to that of I .

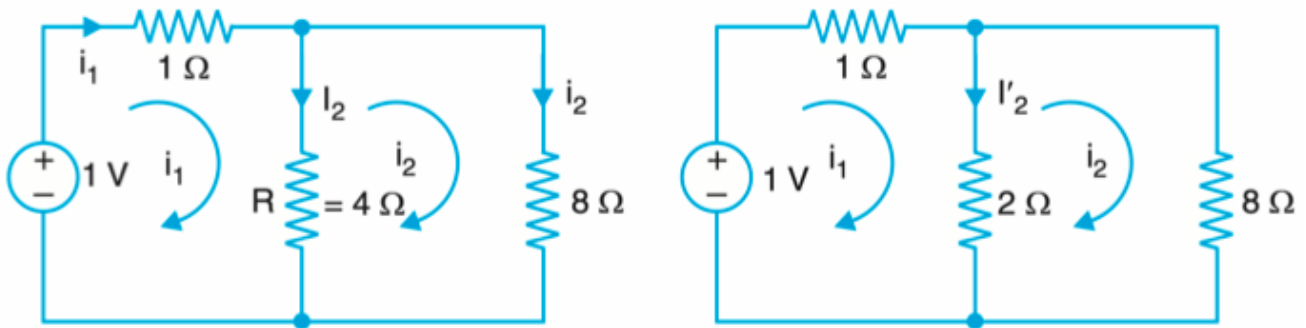Q. In the circuit below, the resistor R is changed from 4Ω to 2Ω . Verify the compensation theorem.



A. For the circuit with $R = 4\Omega$,

$$i_1 = \frac{3}{11} \text{ A}, \quad i_2 = \frac{1}{11} \text{ A} \Rightarrow I_1 = i_1 - i_2 = \frac{2}{11} \text{ A}$$

For the circuit with $R = 2\Omega$,

$$i_1 = \frac{10}{26} \text{ A}, \quad i_2 = \frac{2}{26} \text{ A} \Rightarrow I_2 = i_1 - i_2 = \frac{8}{26} \text{ A}$$


$$\text{Hence, } \delta I = I_2 - I_1 = \frac{18}{143} \text{ A}$$

Using the compensation theorem,


$$V_c = I_2 (\delta Z) = \frac{2}{11} (-2) = -\frac{4}{11} \text{ V}$$

Using the modified circuit,
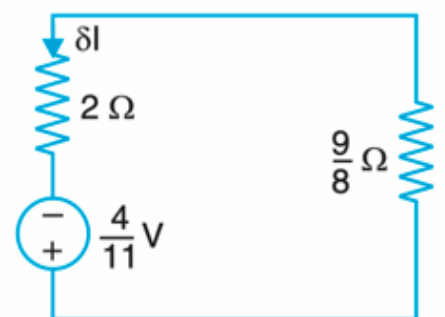
$$\delta I = \frac{\frac{4}{11}}{2 + \frac{8}{9}} = \frac{18}{143} \text{ A}.$$



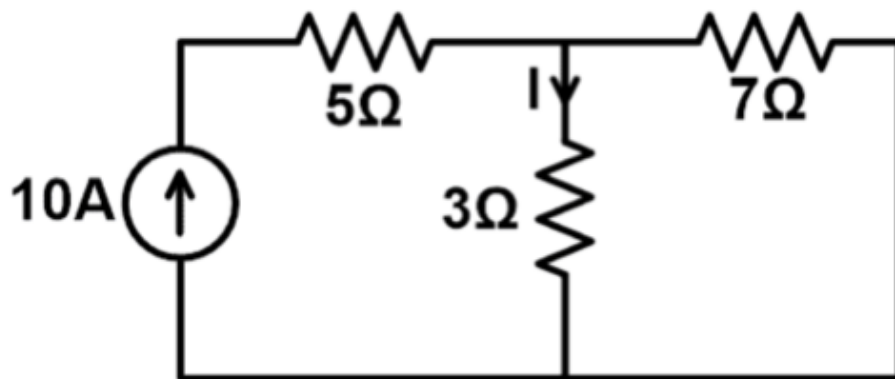Q. Using compensation theorem, find the change in current in the 3Ω resistor if it is replaced by a 7Ω resistor.




A. Across the 3Ω resistor,

$$V_{TH} = 70V, \quad Z_{TH} = \frac{70}{10} = 7\Omega$$

Hence,

$$V_c = \left(\frac{7}{10} \cdot 10 \right) \cdot 4$$

$$= 28V$$

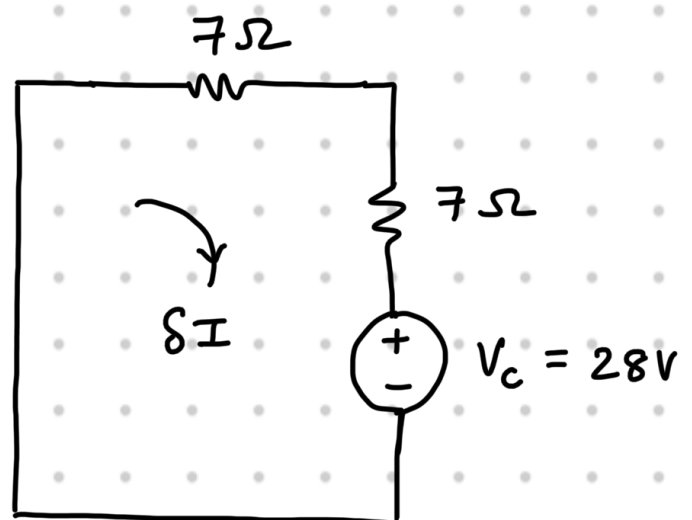

$$\delta I = \frac{-28}{14} = -2A$$


Therefore, change in current = $-2A$

and new current in $3\Omega = 7 - 2 = 5A$

Tellegen's Theorem:

At any given time, the sum of power delivered to each branch of any electric network is zero \equiv Conservation of Power.

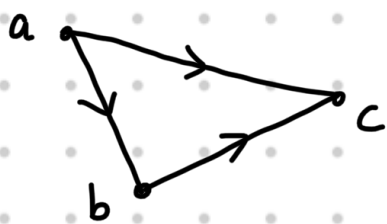
We can easily verify this for a simple three node network:



$$(V_a - V_b) i_{ab} + (V_b - V_c) i_{bc} + (V_a - V_c) i_{ac} = 0$$

Consider an arbitrary network with b branches and n nodes. Let the branch voltages v_1, v_2, \dots, v_b satisfy all the constraints imposed by KVL and the branch currents i_1, i_2, \dots, i_b satisfy all the constraints imposed by KCL. Then the node voltages of the network $e_1, e_2, \dots, e_p, \dots, e_q, \dots, e_n$ are uniquely specified.

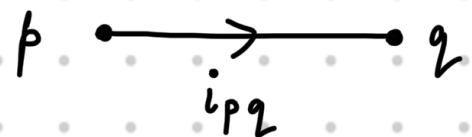Now, let us assume that k^{th} branch connects the nodes p and q and take node 1 as the datum node ($e_1 = 0$).



$$\text{Then, } v_k i_k = (e_p - e_q) i_{pq}$$

For all the b branches,

$$\Rightarrow \sum_{k=1}^b v_k i_k = \frac{1}{2} \sum_{p=1}^n \sum_{q=1}^n (e_p - e_q) i_{pq}$$

$$\Rightarrow \sum_{k=1}^b v_k i_k = \frac{1}{2} \sum_{p=1}^n e_p \sum_{q=1}^n i_{pq} - \frac{1}{2} \sum_{q=1}^n e_q \sum_{p=1}^n i_{pq}$$

According to KCL, $\sum_{q=1}^n i_{pq} = \sum_{p=1}^n i_{pq} = 0$

Therefore, $\sum_{k=1}^b v_k i_k = 0$

Hence, the sum of the power delivered to all branches of a network is zero.


Note: Consider two networks N_1 and N_2 , having the same graph with the same reference directions assigned to the branches of these networks, but with different element values and kinds. Let v_{k_1} and i_{k_1} be the voltages and currents in N_1 and v_{k_2} and i_{k_2} the voltages and currents in N_2 . With all currents and voltages satisfying Kirchhoff's laws, then by

Tellegen's theorem: $\sum_{k=1}^b v_{k_1} i_{k_2} = 0 = \sum_{k=1}^b v_{k_2} i_{k_1}$

Q. Verify Tellegen's theorem for the network shown below. Given :

$$v_0 = 20V, \quad v_1 = 16V, \quad v_2 = \underline{\quad}, \quad v_3 = \underline{\quad}, \quad v_4 = \underline{\quad}, \quad v_5 = 6V$$
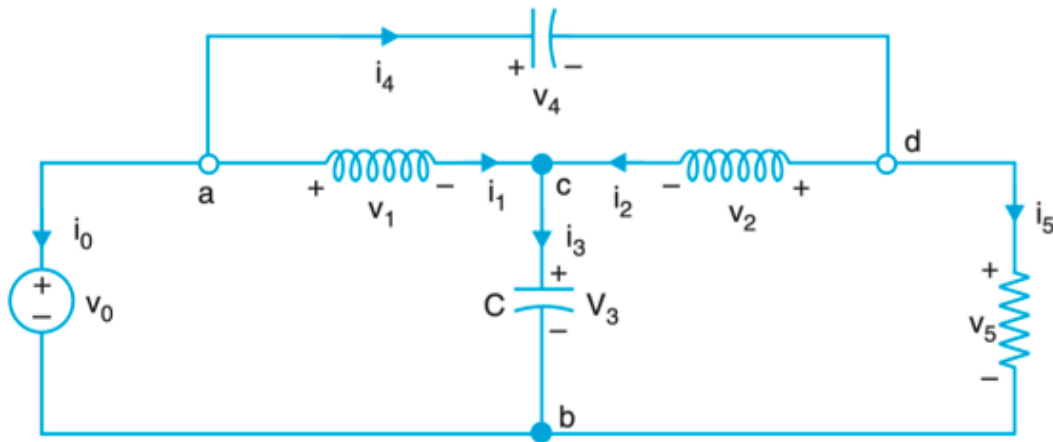
$$i_0 = -16A, \quad i_1 = \underline{\quad}, \quad i_2 = 2A, \quad i_3 = \underline{\quad}, \quad i_4 = 4A, \quad i_5 = \underline{\quad}.$$



A. First, using KCL and KVL find the missing voltages and currents.

Hence,

$$v_0 = 20V, \quad v_1 = 16V, \quad v_2 = \underline{2V}, \quad v_3 = \underline{4V}, \quad v_4 = \underline{14V}, \quad v_5 = 6V$$

$$i_0 = -16A, \quad i_1 = \underline{12A}, \quad i_2 = 2A, \quad i_3 = \underline{14A}, \quad i_4 = 4A, \quad i_5 = \underline{2A}.$$

Now,

$$\sum_{k=0}^5 v_k i_k = 20(-16) + 16(12) + 2(2) + 4(14) + 14(4) + 6(2)$$

$$= 0$$