

Filters

Filters play an integral part in electrical circuits such as radios and TV receivers.

A filter is a circuit that is designed to pass or reject signals with desired frequencies.

There are four types of filters:


- (1). Low-pass filter: Passes low frequencies and stops high frequencies.
- (2). High-pass filter: Passes high frequencies and stops low frequencies.
- (3). Band-pass filter: Passes frequencies within a band and stops frequencies outside that band.
- (4). Band-stop filter: Stops frequencies within a band and passes frequencies outside that band.

Each of these filters can be designed using passive components (R , L , and C) or using active components (opamps and transistors).


Passive Filters : We shall first discuss the four filters using passive components.

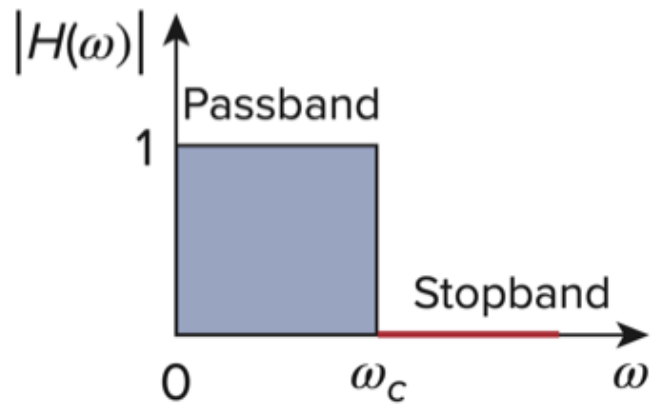1. Low - Pass Filter : An ideal low-pass filter eliminates all frequencies above a designated cut-off frequency.

However, ideal filters are impossible to realize.



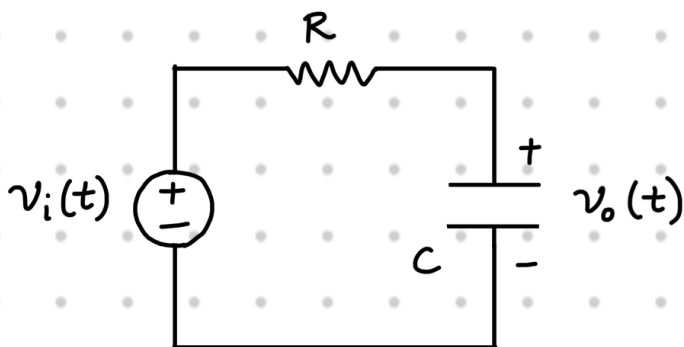A simple RC/RL circuit can be used to build a practical low pass filter.



$$V_o(s) = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} V_i(s)$$

$$\Rightarrow H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC}$$

substituting $s = j\omega$, $H(j\omega) = \frac{1}{1 + j\omega RC}$


$$\Rightarrow |H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Clearly, $H(0) = 1$, $H(\infty) = 0$

The cut-off frequency (ω_c) is defined as the frequency at which the transfer function drops in magnitude to $1/\sqrt{2}$ ($\approx 70.71\%$ of its maximum value). Hence,

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}}$$

$$\Rightarrow \omega_c = \frac{1}{RC}$$

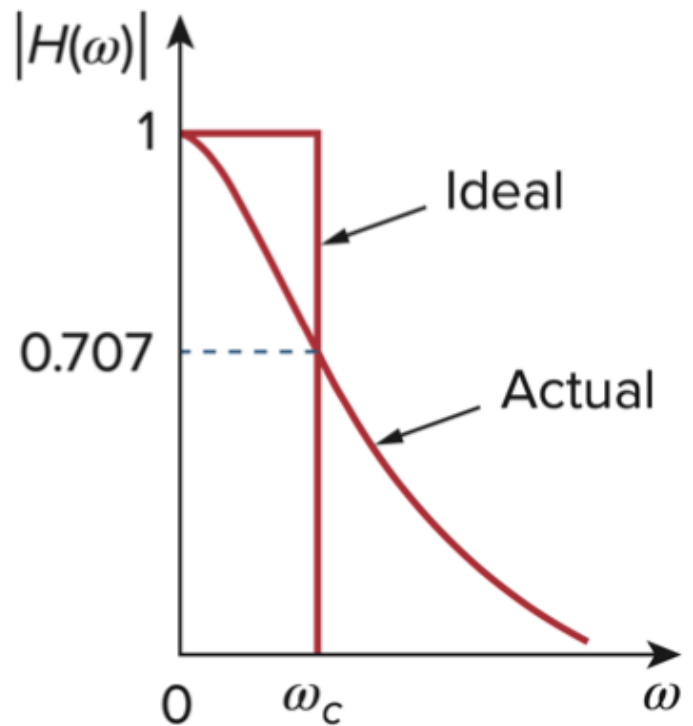



Note: In communication systems, gain is measured in decibels.

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1} = 20 \log_{10} \frac{V_2}{V_1}$$

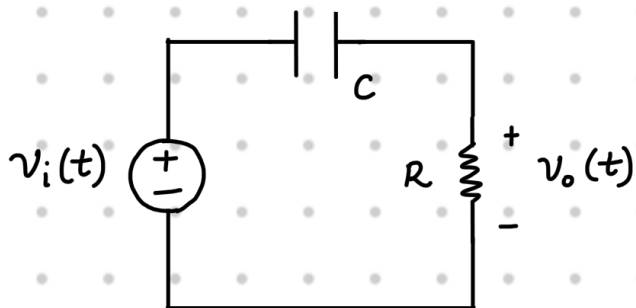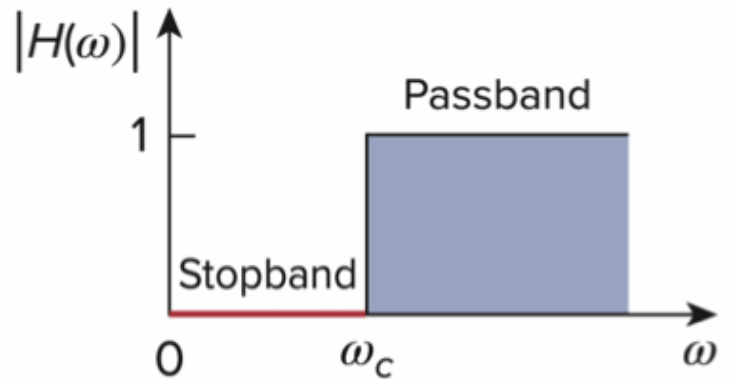2. High-Pass Filter: A high-pass filter eliminates all frequencies below a designated cut-off frequency.

A simple CR circuit

can be used to build a practical high pass filter.



$$V_o(s) = \frac{R}{R + \frac{1}{Cs}} V_i(s)$$

$$\Rightarrow H(s) = \frac{V_o(s)}{V_i(s)} = \frac{sRC}{1 + sRC}$$


$$\Rightarrow |H(j\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Clearly, $H(0) = 0$

and $H(\infty) = 1$



Again, the cut-off frequency

is $\omega_c = \frac{1}{RC}$.

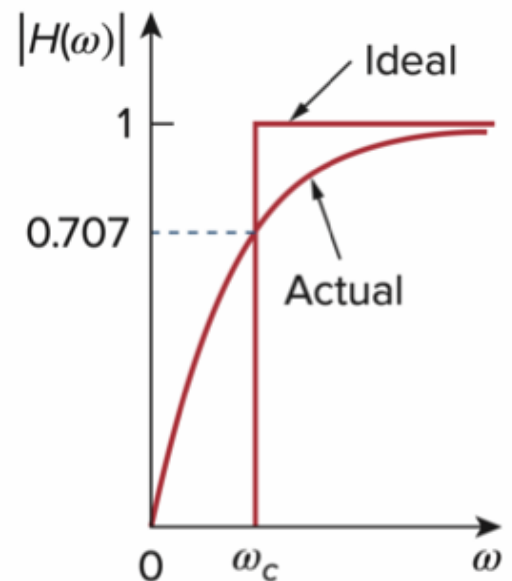

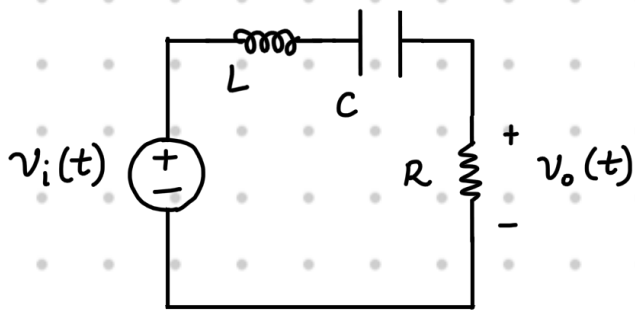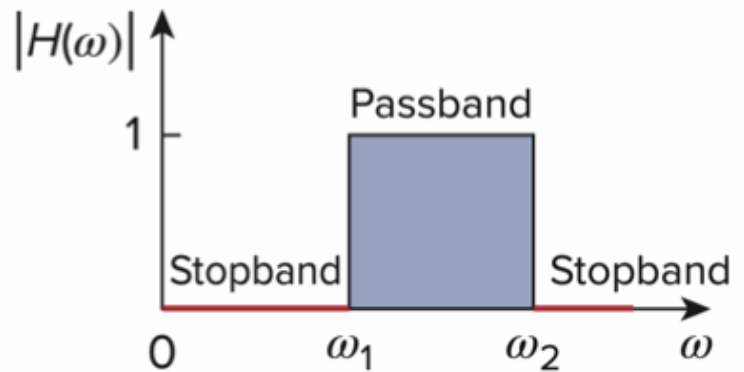3. Band-Pass Filter : A band-pass filter passes frequencies within a frequency band and blocks frequencies outside the band.

A series RLC circuit can be used to build a practical band-pass filter.




$$V_o(s) = \frac{R}{R + \frac{1}{sC} + sL} V_i(s)$$

$$\Rightarrow |H(j\omega)| = \frac{R}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

Clearly, $H(0) = H(\infty) = 0$

The center frequency where $|H(j\omega)| = 1$ is :



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

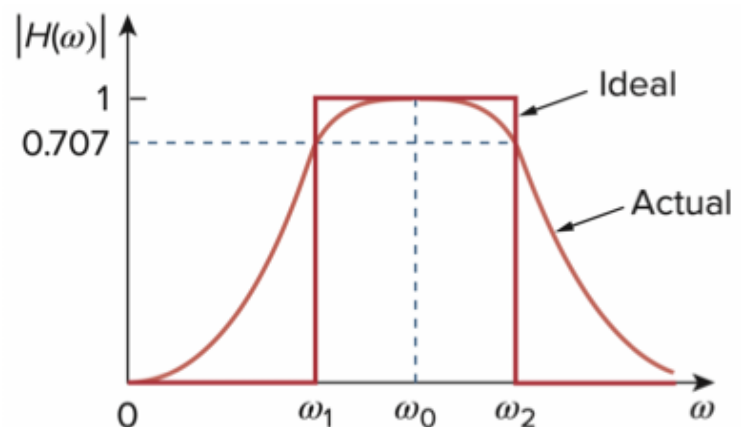

and $B = \omega_2 - \omega_1$ is called as the bandwidth of passband.

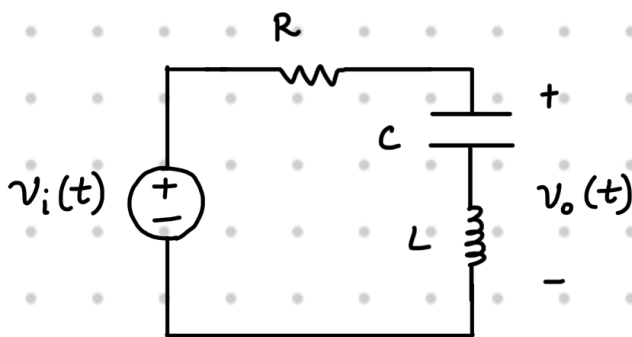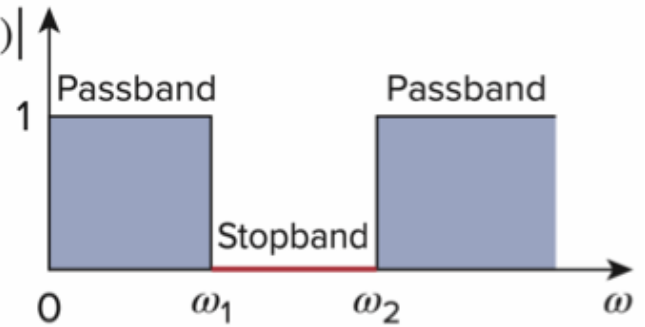4. Band-Stop Filter : A band-stop filter stops frequencies within a frequency band and passes frequencies outside the band.

A series RLC circuit can be used to build a practical band-stop filter.




$$V_o(s) = \frac{sL + \frac{1}{sC}}{R + \frac{1}{sC} + sL} V_i(s)$$

$$\Rightarrow |H(j\omega)| = \frac{(\omega L - 1/\omega C)}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

Clearly, $H(0) = H(\infty) = 1$

The center frequency where $|H(j\omega)| = 0$ is :

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

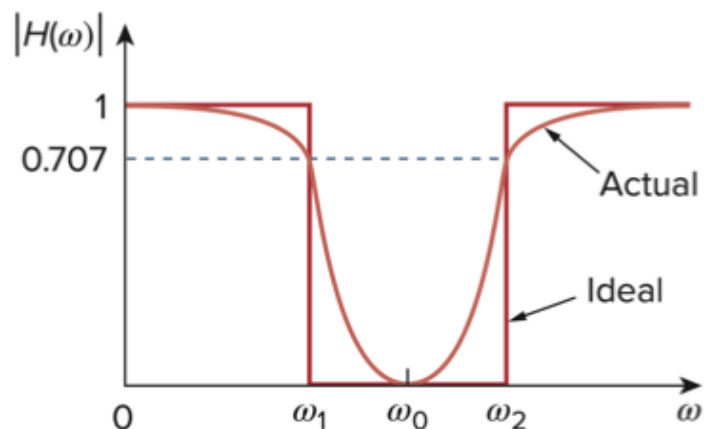

and $B = \omega_2 - \omega_1$ is called as the bandwidth of rejection.

NOTE : As discussed in the class, ideal filter characteristics will force the impulse response $h(t)$ to be non-zero for $t < 0$.

We will now show that for a system to be causal, $h(t)$ should be equal to zero for $t < 0$.

$$y(t) = x(t) * h(t) = \int_{-\infty}^{\infty} x(\tau) h(t-\tau) d\tau$$

$$\Rightarrow y(t_0) = \int_{-\infty}^{\infty} x(\tau) h(t_0-\tau) d\tau$$

$$\Rightarrow y(t_0) = \int_{-\infty}^{t_0} x(\tau) h(t_0-\tau) d\tau + \int_{t_0}^{\infty} x(\tau) h(t_0-\tau) d\tau$$

For causality, $y(t_0)$ should only depend on $x(t)$ for $t < t_0$

\Rightarrow This term should be zero.

$$\Rightarrow h(t_0-\tau) < 0 \text{ for } \tau > t_0$$

substituting $t_0 - \tau = t$ gives

$$h(t) < 0 \text{ for } t < 0 \quad \underline{\underline{\text{QED.}}}$$