


## Interconnection of Two-Port Networks

A complex two-port network can be designed by interconnecting simple two-port networks.

We will study three types of connections: Cascade, Series, and Parallel.
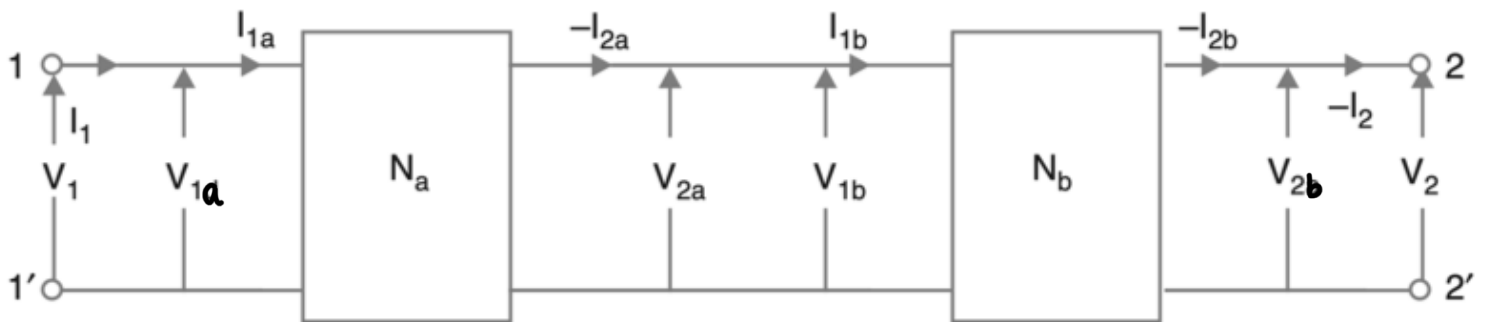
### Cascade Connection:

Two networks are said to be connected in cascade if the output port of the first becomes the input port of the second as shown below.



Using ABCD / transmission parameters:

$$\text{for } N_a : \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

and for  $N_b$  : 
$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Now, for the entire network,

let 
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

but 
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$


$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Hence, 
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

Therefore, the overall transmission parameter matrix is the product of the transmission parameter matrices of each network in the cascade.
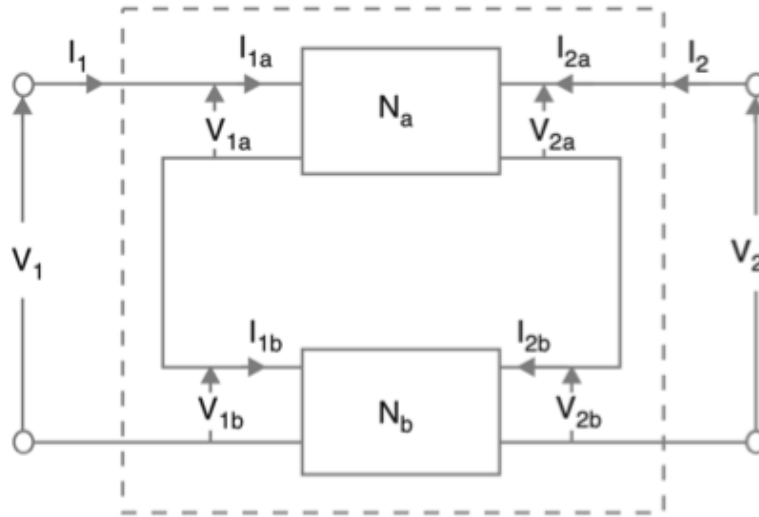
## Series Connection :

Two networks are said to be connected in series if they are connected as shown below.



Using  $Z$ -parameters will be helpful in characterizing series connections.

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} z_{11a} & z_{12a} \\ z_{21a} & z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} z_{11b} & z_{12b} \\ z_{21b} & z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$


$$\text{Clearly, } V_1 = V_{1a} + V_{1b} = (z_{11a} + z_{11b}) I_1 + (z_{12a} + z_{12b}) I_2$$

$$V_2 = V_{2a} + V_{2b} = (z_{21a} + z_{21b}) I_1 + (z_{22a} + z_{22b}) I_2$$

Hence, 
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11a} + z_{11b} & z_{12a} + z_{12b} \\ z_{21a} + z_{21b} & z_{22a} + z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Therefore, the overall impedance parameter matrix is the sum of the impedance parameter matrices of each network connected in series

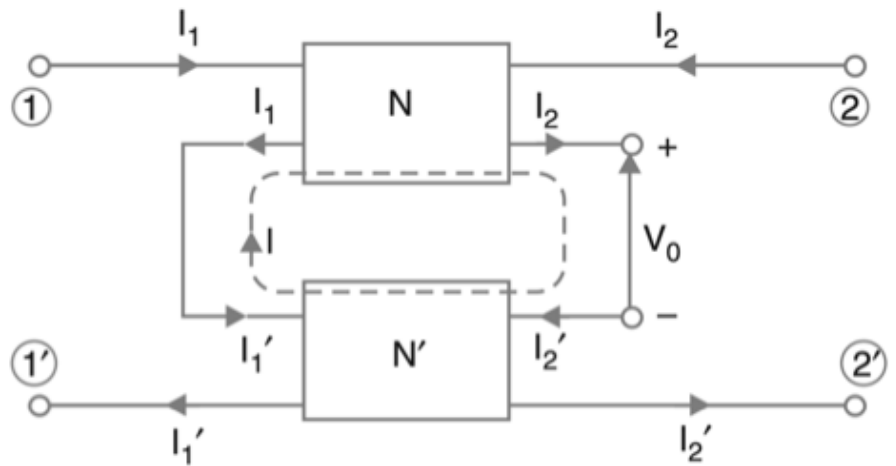
Note: Two networks  $N$  and  $N'$  can be connected in series only if  $V_0 = 0$  as shown below.



If  $V_0 \neq 0$ , there will be circulating current which will imply that the current entering one terminal of port 2 will not be equal to the current leaving the other terminal.
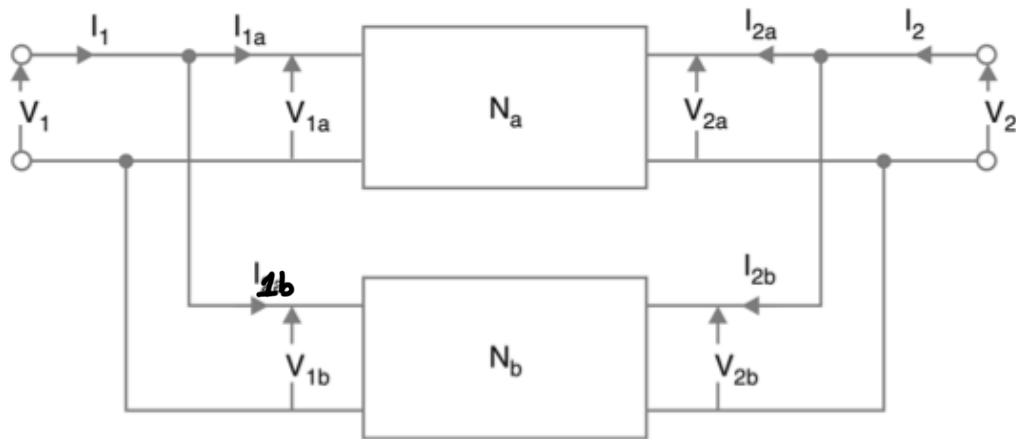
## Parallel Connection :

Two networks are said to be connected in parallel if they are connected as shown below.



Using  $\gamma$ -parameters will be helpful in characterizing parallel connections.

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} \gamma_{11a} & \gamma_{12a} \\ \gamma_{21a} & \gamma_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} \gamma_{11b} & \gamma_{12b} \\ \gamma_{21b} & \gamma_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$


$$\text{Clearly, } I_1 = I_{1a} + I_{1b} = (\gamma_{11a} + \gamma_{11b}) V_1 + (\gamma_{12a} + \gamma_{12b}) V_2$$

$$I_2 = I_{2a} + I_{2b} = (\gamma_{21a} + \gamma_{21b}) V_1 + (\gamma_{22a} + \gamma_{22b}) V_2$$

Hence, 
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Therefore, the overall admittance parameter matrix is the sum of the admittance parameter matrices of each network connected in parallel.

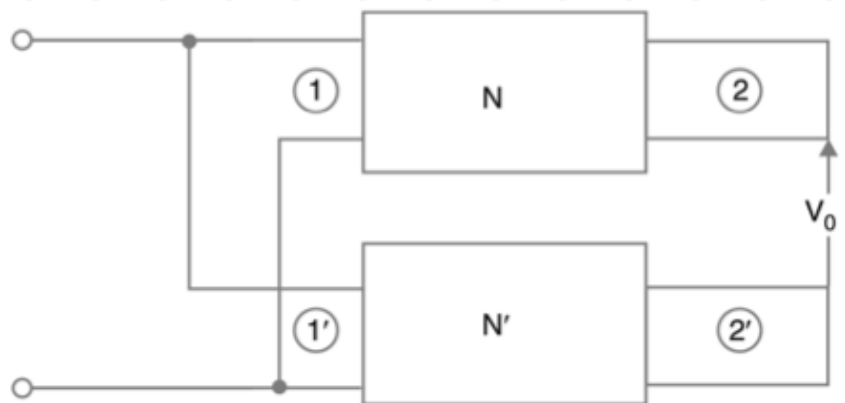Note: Two networks  $N$  and  $N'$  can be connected in parallel only if  $V_0 = 0$  as shown below.



In the circuit, ports 1 and 1' are connected together and ports 2 and 2' are short-circuited individually. If  $V_0 \neq 0$ , it will imply that the output terminals of the connected network are not short-circuited.