

## Assignment - 2

EEEC201 - Signals, Systems, and Networks (Monsoon 2024)

Department of Electrical Engineering, IIT (ISM) Dhanbad

Due: 24.10.2024

1. Find the Laplace Transforms of the following (attempt ANY eight):

(a)  $(t + e^{-t} + t^2 e^{-t} + (t - 4)e^{2t})u(t)$  (b)  $(\sin^2 t)u(t)$  (c)  $\frac{\sin kt}{t}u(t)$

(d)  $\cosh(t + \theta)u(t)$  (e)  $(1 - (1 - t)e^{-3t})u(t)$  (f)  $|t|e^{-|t|}$

(g)  $x(t) = \begin{cases} t & 0 \leq t < 1 \\ e^t & t \geq 1 \\ 0 & \text{else} \end{cases}$  (h)  $x(t) = \begin{cases} t - \pi & \pi \leq t < 2\pi \\ 0 & \text{else} \end{cases}$  (i)  $(t \sin t) u(t)$

(j)  $x(t) = \begin{cases} 1 & 0 \leq t < 2 \\ t^2 - 4t + 4 & t \geq 2 \\ 0 & \text{else} \end{cases}$  (k)  $x(t) = \begin{cases} \cos(\pi t) & 0 < t < 4 \\ 0 & \text{else} \end{cases}$

2. Find the Inverse Laplace Transforms of the following (attempt ANY eight):

(a)  $\frac{24}{s^4} - \frac{9}{s^2 + 9}$  (b)  $\frac{8}{s^3 + 4s}$  (c)  $\frac{1 + e^{-2s}}{s^2 + 6}$  (d)  $\frac{2s + 3}{s^2 + 4s + 13}$

(e)  $\frac{1}{(s + 1)(s^2 - 1)}$  (f)  $\frac{s^2 - 2s}{s^4 + 5s^2 + 4}$  (g)  $\frac{e^{-3s}}{s - 2}$  (h)  $\frac{5(s + 2)^2}{s(s + 1)^3}$

(i)  $\frac{2s + 5}{s^2 + 5s + 6}e^{-2s}$  (j)  $\frac{s}{(s - 3)^5}$  (k)  $\frac{3 + e^{-(s-1)}}{s^2 - 2s + 5}$  (l)  $\frac{9 + s}{4 - s^2}$

3. Verify the Initial value theorem and the Final value theorem for the following (attempt all):


(a)  $e^{-t}(t + 2)^2 u(t)$  (b)  $(1 + e^{-t}(\sin t + \cos t)) u(t)$   
(c)  $t^2 e^{-3t} u(t)$  (d)  $u(t - T)$

4. Solve the following differential equations (attempt ANY six):


(a)  $y' + 3y = t^2 e^{-3t} + t e^{-2t} + t$  with  $y(0) = 1$   
(b)  $y'' + 4y = 0$  with  $y(0) = 1, y'(0) = 6$   
(c)  $y'' + 4y' + 8y = e^{-t}$  with  $y(0) = y'(0) = 0$   
(d)  $y''' - y' = 2$  with  $y(0) = y'(0) = y''(0) = 4$   
(e)  $y'' + 2y' + 5y = 0$  with  $y(0) = 2, y'(0) = 0$   
(f)  $y'' + 4y' + 3y = 10\cos(t)$  with  $y(0) = 1, y'(0) = 2$   
(g)  $y'' + 4y' + 4y = 3te^{-2t}$  with  $y(0) = 0, y'(0) = 1$   
(h)  $y'''' + y = 0$  with  $y(0) = y'(0) = y''(0) = y'''(0) = 1$

5. Using KCL/KVL and Nodal/Mesh Analysis, answer the following (attempt ANY twenty):

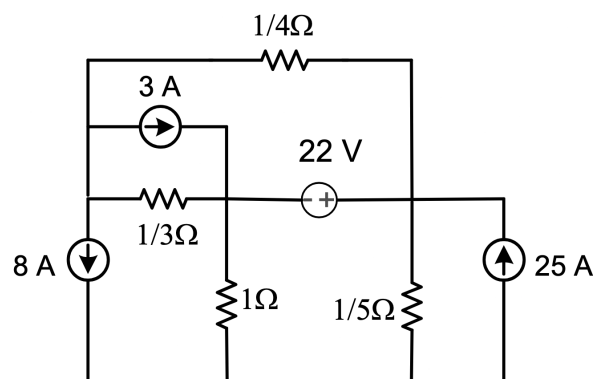
(a) What are the node voltages in this circuit?



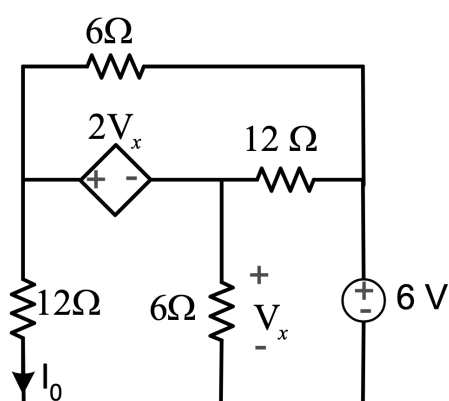
(b) Calculate the node voltages and the current  $I_0$  in the circuit below:



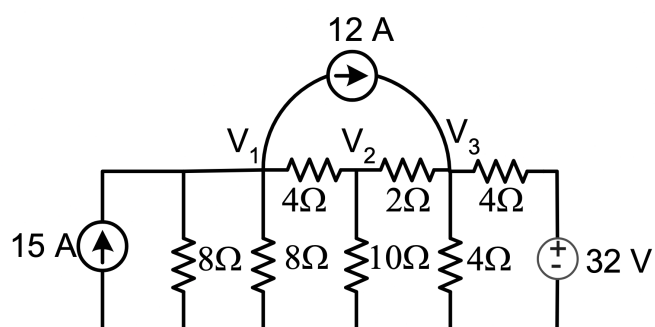
(c) What is the power dissipated by the 10 Ohm resistor?



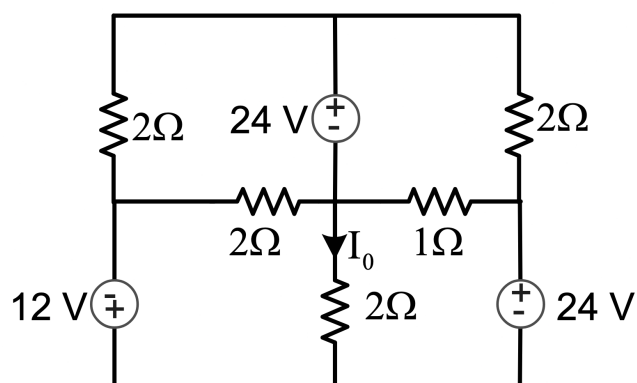
(d) Calculate the current  $I_0$  in the circuit:



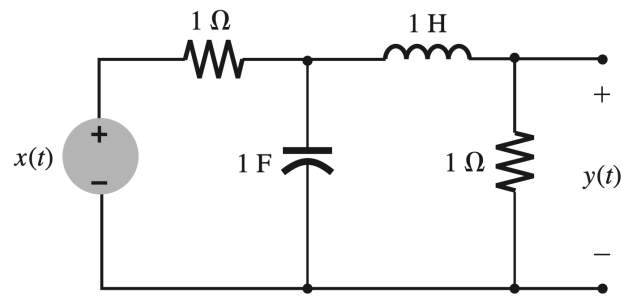
(e) If  $x(t) = te^{-t}u(t)$ , calculate  $y(t)$ :



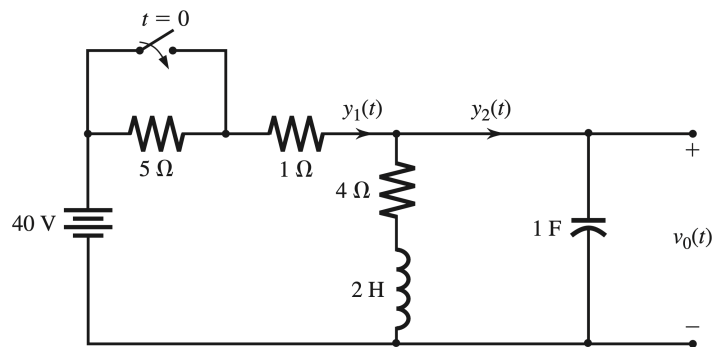
(f) If the switch is open for a long time and suddenly closed at  $t = 0$ , calculate  $y_1(t)$  and  $y_2(t)$ :



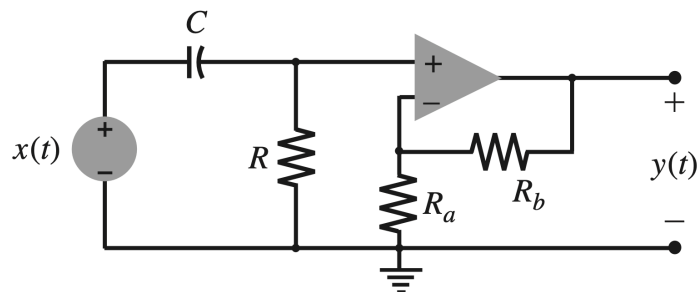
(g) What is the transfer function of this circuit?



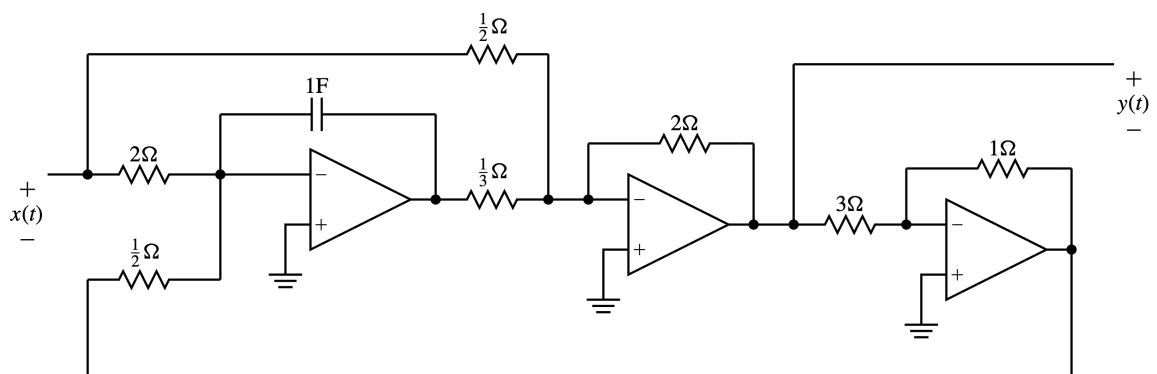(h) What is the transfer function of this circuit?




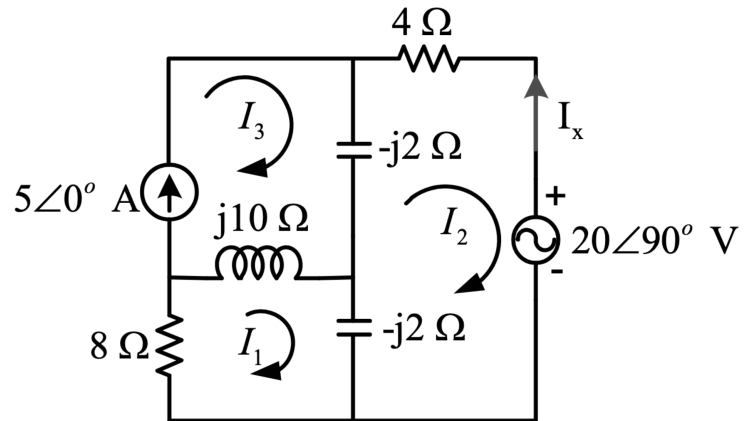(i) What is the current  $I_x$  flowing out of the voltage source?




(j) What is the voltage  $v_o(t)$  across the capacitor?

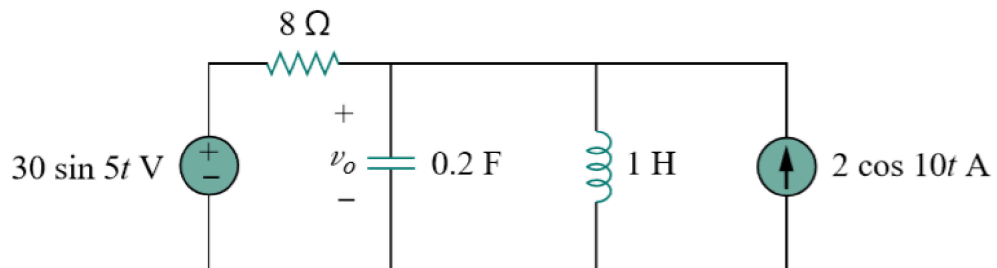
(Hint: Convert the circuit to phasor domain, solve the equations and convert back to the time domain)



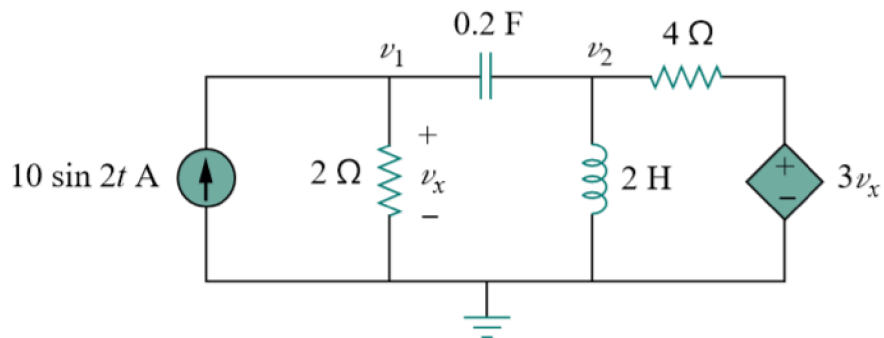(k) What are the node voltages  $v_1(t)$  and  $v_2(t)$ ?




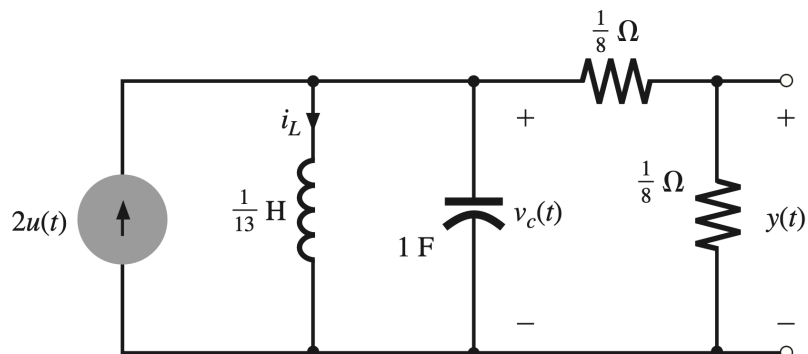(l) If  $i_L(0^-) = 1A$  and  $v_C(0^-) = 3V$ , calculate the voltage  $y(t)$  for  $t \geq 0$ .




(m) Assuming zero initial conditions and  $\omega_0^2 = \frac{1}{LC}$ , calculate the current  $y(t)$  if

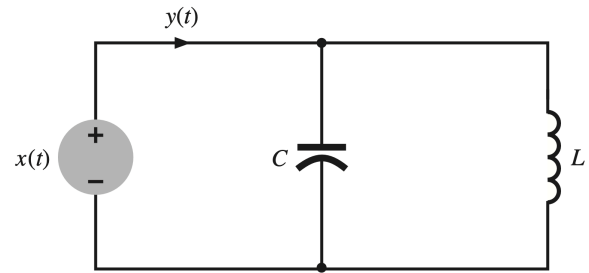
$$x(t) = (A \sin \omega_0 t + B \cos \omega_0 t)u(t)$$



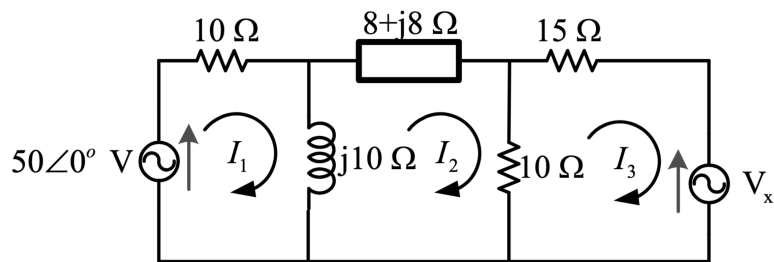
(n) What should be the value of  $V_x$  so that no current flows through the impedance  $8 + j8$ ?



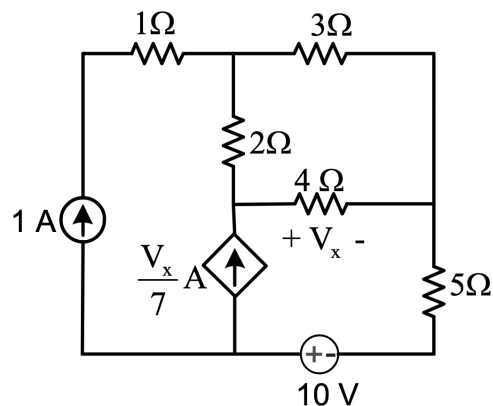
(o) What is the power dissipated or supplied by the voltage source?



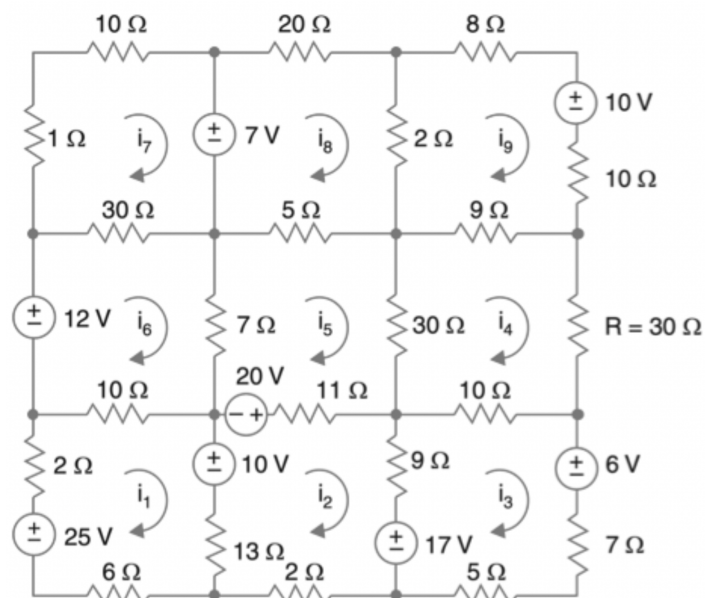
(p) What is the power dissipated by the 30 Ohm resistor?



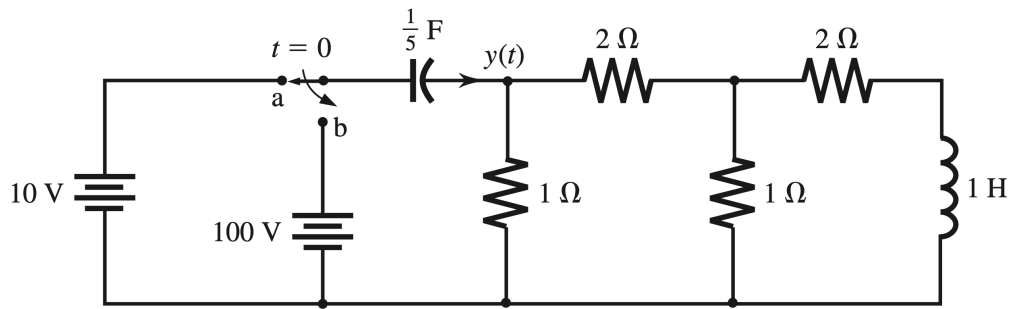
(q) If the switch is at “a” for a long time and suddenly moved to “b” at  $t = 0$ , calculate  $y(t)$ :



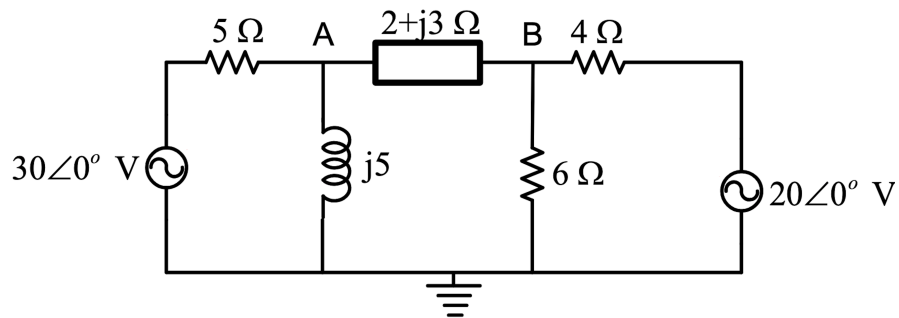
(r) What is the current flowing through the 6 Ohm resistor?



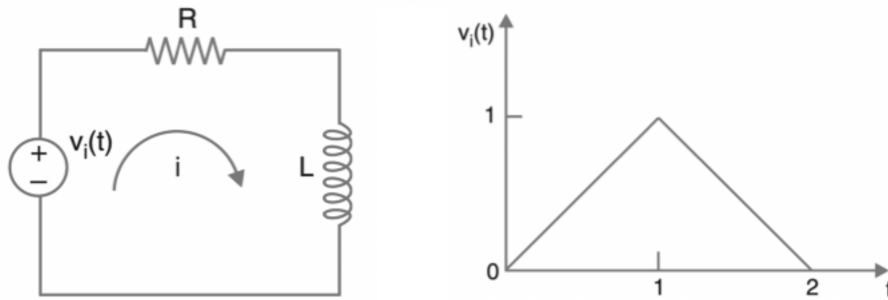
(s) Assuming zero initial conditions and  $R = 2$  Ohms and  $L = 2$  H, calculate the current  $i(t)$  in the circuit:



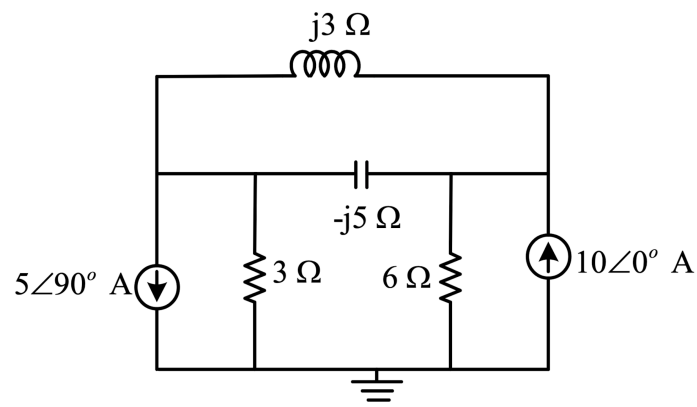
(t) What is the voltage across the 6 Ohm resistor?



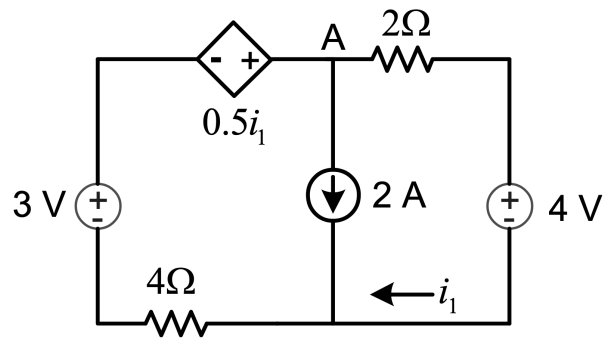(u) Calculate the current flowing through the 4 Ohm resistor:



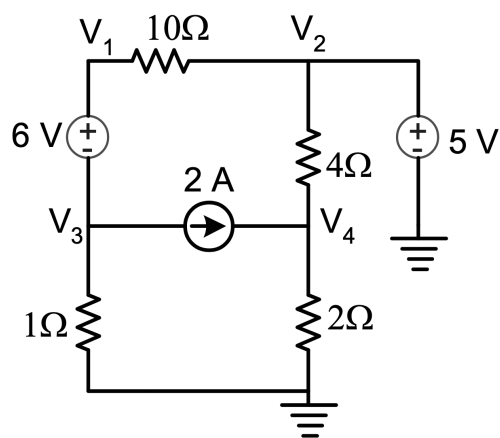(v) Calculate all the node voltages in the circuit below:



(w) Calculate the current  $i$  in the circuit below:

